

COC2072 – Digital Logic and System Design


Prof. M. M. Sufyan Beg

Department of Computer Engineering


Z. H. College of Engineering & Technology

Aligarh Muslim University, India

Unit III – Sequential Circuits

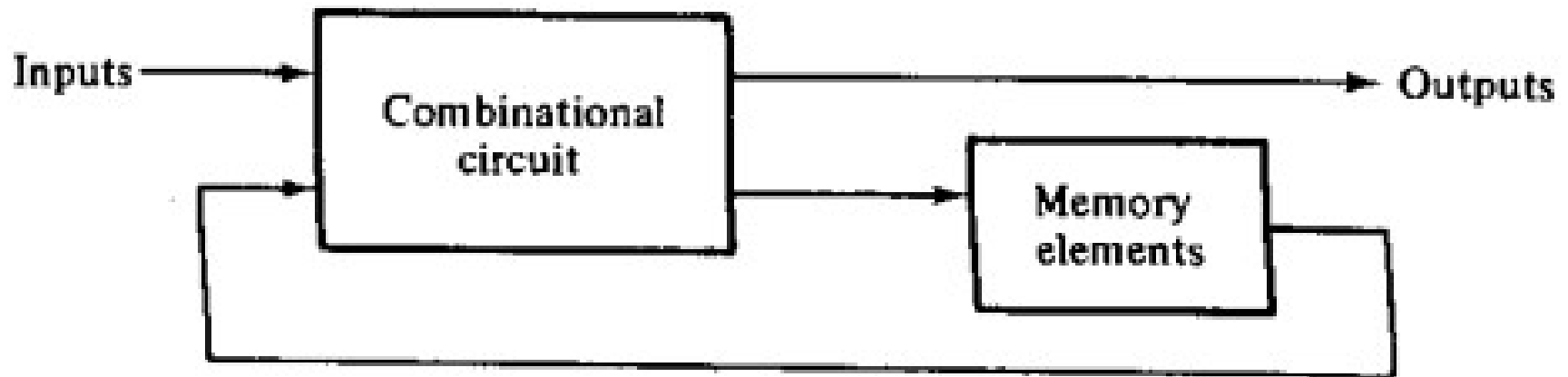


Basic Flip-Flop Circuit with NOR Gates

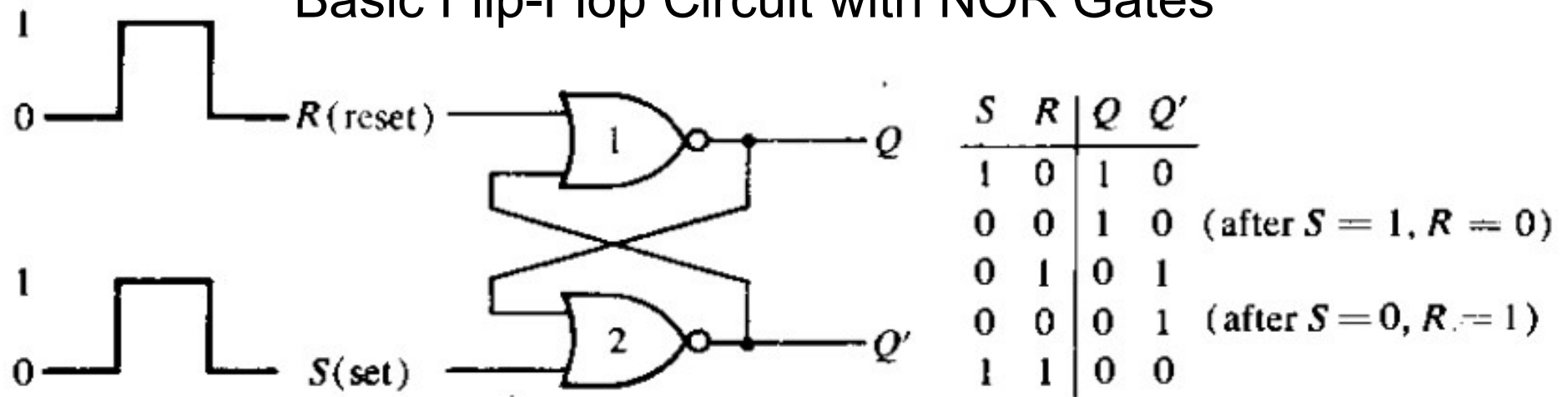


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Basic Flip-Flop Circuit with NAND Gates

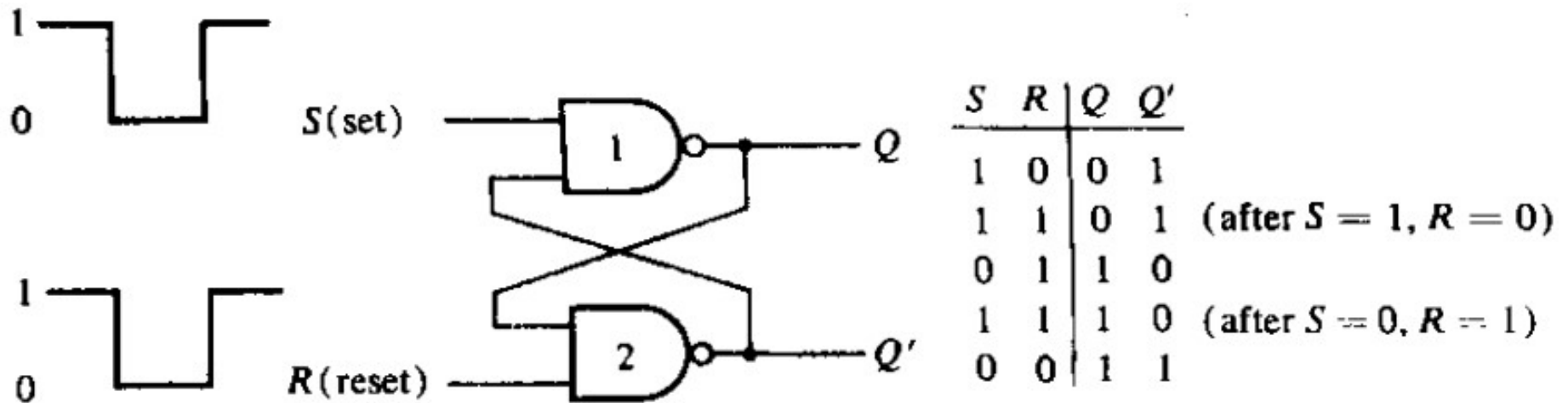

Clocked RS Flip-Flop

 

Q	S	R	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate


Characteristic table

	SR			
Q	00	01	11	10
0			X	1
1	1		X	1

$$Q(t+1) = S + R'Q$$



$$SR = 0$$

Characteristic equation

 

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	Indeterminate

D Flip-Flop

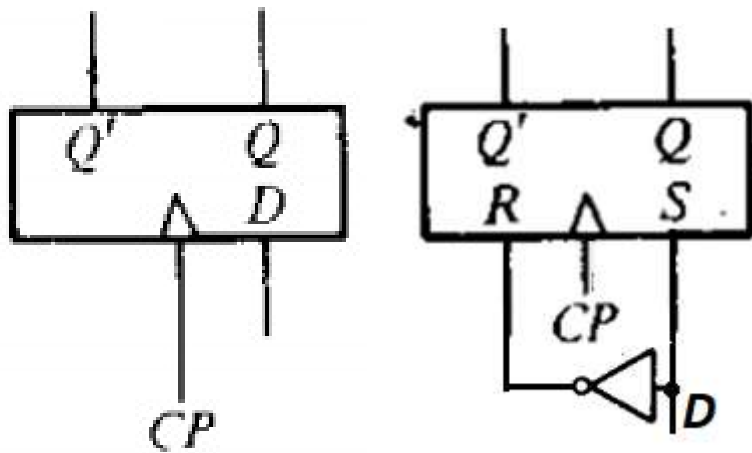 

Q	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

	0	1
0		1
1		1




$$Q(t+1) = D$$

Characteristic table Characteristic equation



RS Flip-Flop and D Flip-Flop

S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	Indeterminate

D	$Q(t+1)$
0	0
1	1

   

JK Flip-Flop

  

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q(t)'$

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0




Characteristic table

		JK			
		00	01	11	10
Q	0			1	1
	1	1			1

$$Q(t+1) = JQ' + K'Q$$

Characteristic Equation

T Flip-Flop

   

T	$Q(t+1)$
0	$Q(t)$
1	$Q(t)'$

Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0


Characteristic table

T	0	1
Q		
0		1
1	1	

$$Q(t+1) = TQ' + T'Q$$

Characteristic equation


Binary Ripple Counter

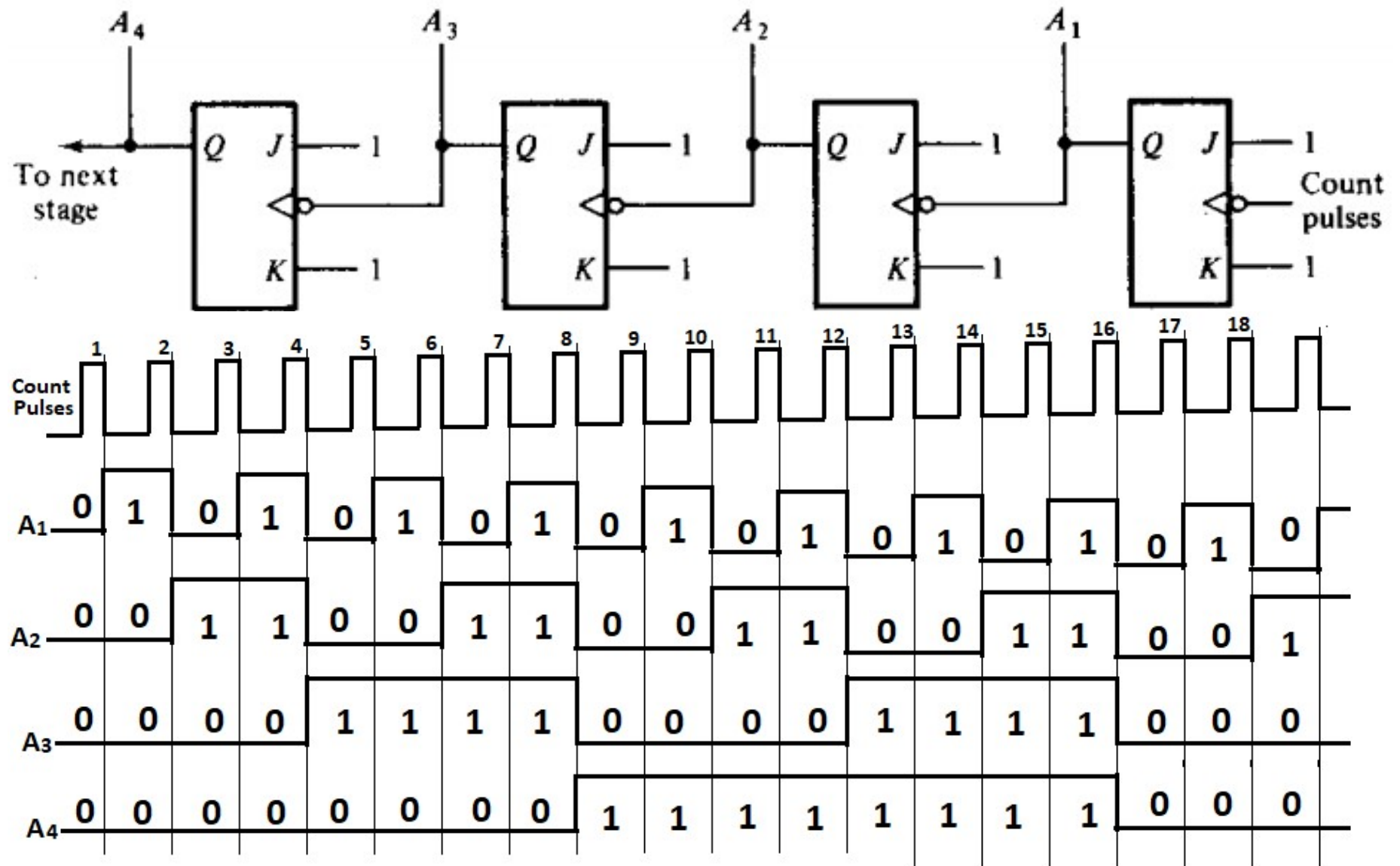

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI


Master-Slave Flip-Flop

- Race Around Condition in JK FF

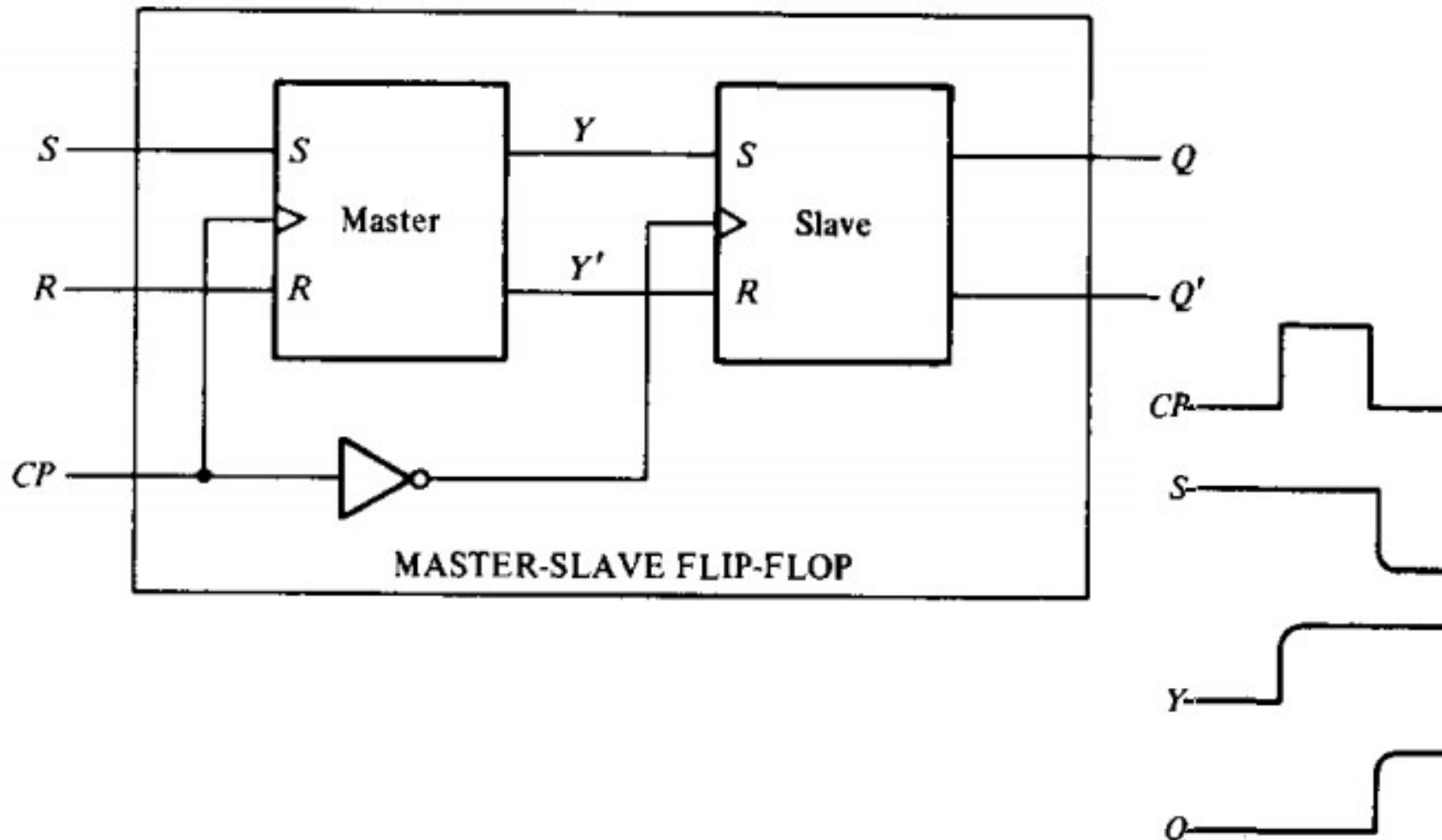

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Clocked Master-Slave JK Flip-Flop

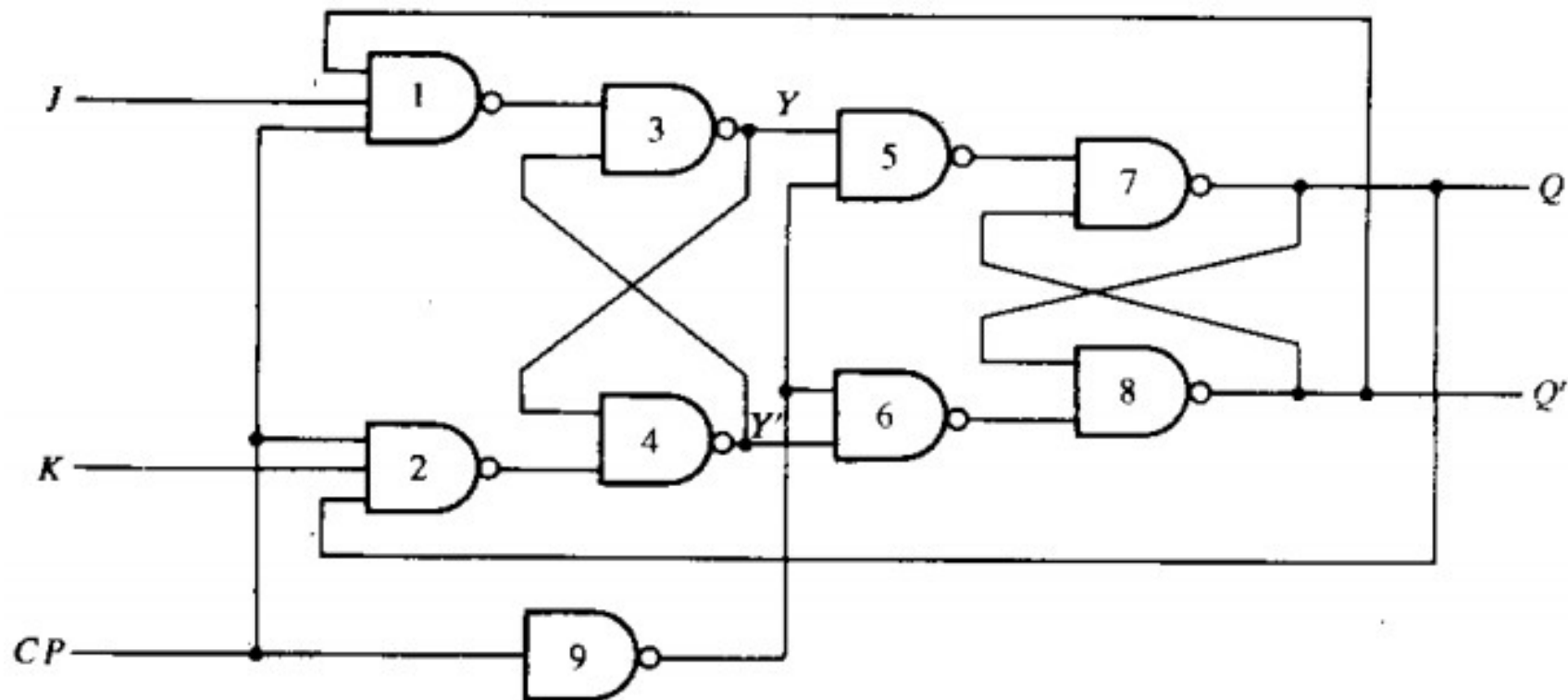

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Flip-Flop Excitation Tables

S	R	$Q(t + 1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	?

Characteristic Table

D	$Q(t + 1)$
0	0
1	1

$Q(t)$	$Q(t + 1)$	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Excitation Table

$Q(t)$	$Q(t + 1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Flip-Flop Excitation Tables (contd.)

J	K	$Q(t + 1)$	$Q(t)$	$Q(t + 1)$	J	K
0	0	$Q(t)$	0	0	0	X
0	1	0	0	1	1	X
1	0	1	1	0	X	1
1	1	$Q'(t)$	1	1	X	0


Characteristic Table

T	$Q(t + 1)$
0	$Q(t)$
1	$Q'(t)$

Excitation Table

$Q(t)$	$Q(t + 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Sequential Circuit Design Using RS-FF

 

Present State	Next state		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
AB	AB	AB	y	y
00	00	01	0	0
01	11	01	0	0
10	10	00	0	1
11	10	11	0	0

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Sequential Circuit Design Using RS-FF (contd.)

Present State		Input	Next State		Required Flip-Flop Inputs				Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>SA</i>	<i>RA</i>	<i>SB</i>	<i>RB</i>	<i>Y</i>
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	0	0
0	1	0	1	1	1	0	X	0	0
0	1	1	0	1	0	X	X	0	0
1	0	0	1	0	X	0	0	X	0
1	0	1	0	0	0	1	0	X	1
1	1	0	1	0	X	0	0	1	0
1	1	1	1	1	X	0	X	0	0

<i>Bx</i>	00	01	11	10
<i>A</i>				
0				1
1	X		X	X

$$SA = Bx'$$

<i>Bx</i>	00	01	11	10
<i>A</i>				
0		1	X	X
1			X	

$$SB = A'x$$

<i>Q(t)</i>	<i>Q(t + 1)</i>	<i>S</i>	<i>R</i>
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

<i>Bx</i>	00	01	11	10
<i>A</i>				
0	X	X	X	
1		1		

$$RA = B'x$$

<i>Bx</i>	00	01	11	10
<i>A</i>				
0	X			
1	X	X		1


$$RB = Ax'$$

<i>Bx</i>	00	01	11	10
<i>A</i>				
0				
1		1		

$$y = AB'x$$

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

 Sequential Circuit Design Using RS-FF (contd.)




$$SA = Bx'$$

$$RA = B'x$$


$$SB = A'x$$

$$RB = Ax'$$

$$y = AB'x$$

 

Sequential Circuit Design Using JK-FF

 

State table

Present state		Next state			
		$x = 0$		$x = 1$	
A	B	A	B	A	B
0	0	0	0	0	1
0	1	1	0	0	1
1	0	1	0	1	1
1	1	1	1	0	0

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI


Sequential Circuit Design Using JK-FF (contd.)

Excitation table

Inputs of combinational circuit			Next state	Outputs of combinational circuit				
Present state		Input		Flip-flop inputs				
<i>A</i>	<i>B</i>			<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>	
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Block Diagram of the Sequential Circuit

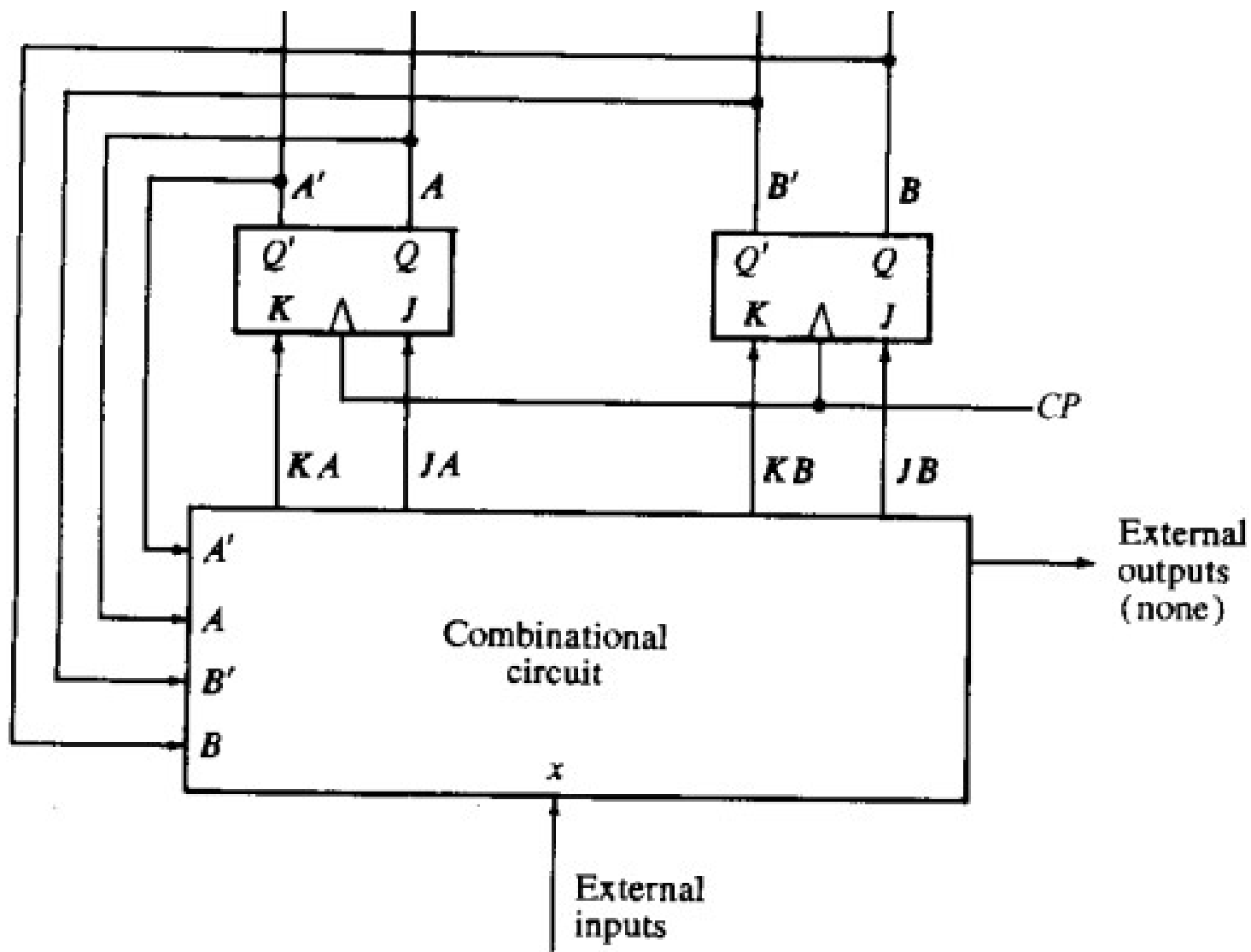

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Maps for the Combinational Circuit

		Bx		B
		00	01	11 10
A	0			1
A	1	X	X	X

$\underbrace{\hspace{10em}}_x$

$$JA = Bx'$$

X	X	X	X
		1	

$$KA = Bx$$


	1	X	X
	1	X	X

$$JB = x$$

X	X		1
X	X	1	

$$KB = A \odot x$$


Logic Diagram of the Sequential Circuit

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

3-bit Binary Counter


State diagram of a 3-bit binary counter

 

Excitation table for a 3-bit binary counter

Count sequence			Flip-flop inputs		
A_2	A_1	A_0	TA_2	TA_1	TA_0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	0	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	1	1	1


3-bit Binary Counter (contd.)

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Self Starting Counters

 - A counter that can start from any state, but eventually reaches the normal count sequence



$Q(t)$	$Q(t + 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present Count State			Next Count State			Required Flip-Flop Inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	0	0	0	X	1	X	1	X	1

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

K-Maps for the Self Starting Counter

A \ BC	00	01	11	10
	0	1	3	2
0			1	1
1	X	X	X	X

$$JA = B$$

A \ BC	00	01	11	10
	0	1	3	2
0	X	X	X	X
1			1	1

$$KA = B$$

A \ BC	00	01	11	10
	0	1	3	2
0		1	X	X
1		1	X	X

$$JB = C$$

A \ BC	00	01	11	10
	0	1	3	2
0	X	X	1	1
1	X	X	1	1

$$KB = 1$$

A \ BC	00	01	11	10
	0	1	3	2
0	1	X	X	
1	1	X	X	

$$JC = B'$$

A \ BC	00	01	11	10
	0	1	3	2
0	X	1	1	X
1	X	1	1	X


$$KC = 1$$

Logic Diagram for the Self Starting Counter

$$JA = B \quad KA = B$$

$$JB = C \quad KB = 1$$


$$JC = B' \quad KC = 1$$

 


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Registers

 A *register* is a group of binary storage cells suitable for holding binary information. A group of flip-flops constitutes a register, since each flip-flop is a binary cell capable of storing one bit of information. An n -bit register has a group




4-bit Register with Parallel Load

 


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Register with Parallel Load Using D-FF

 


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Shift Registers

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

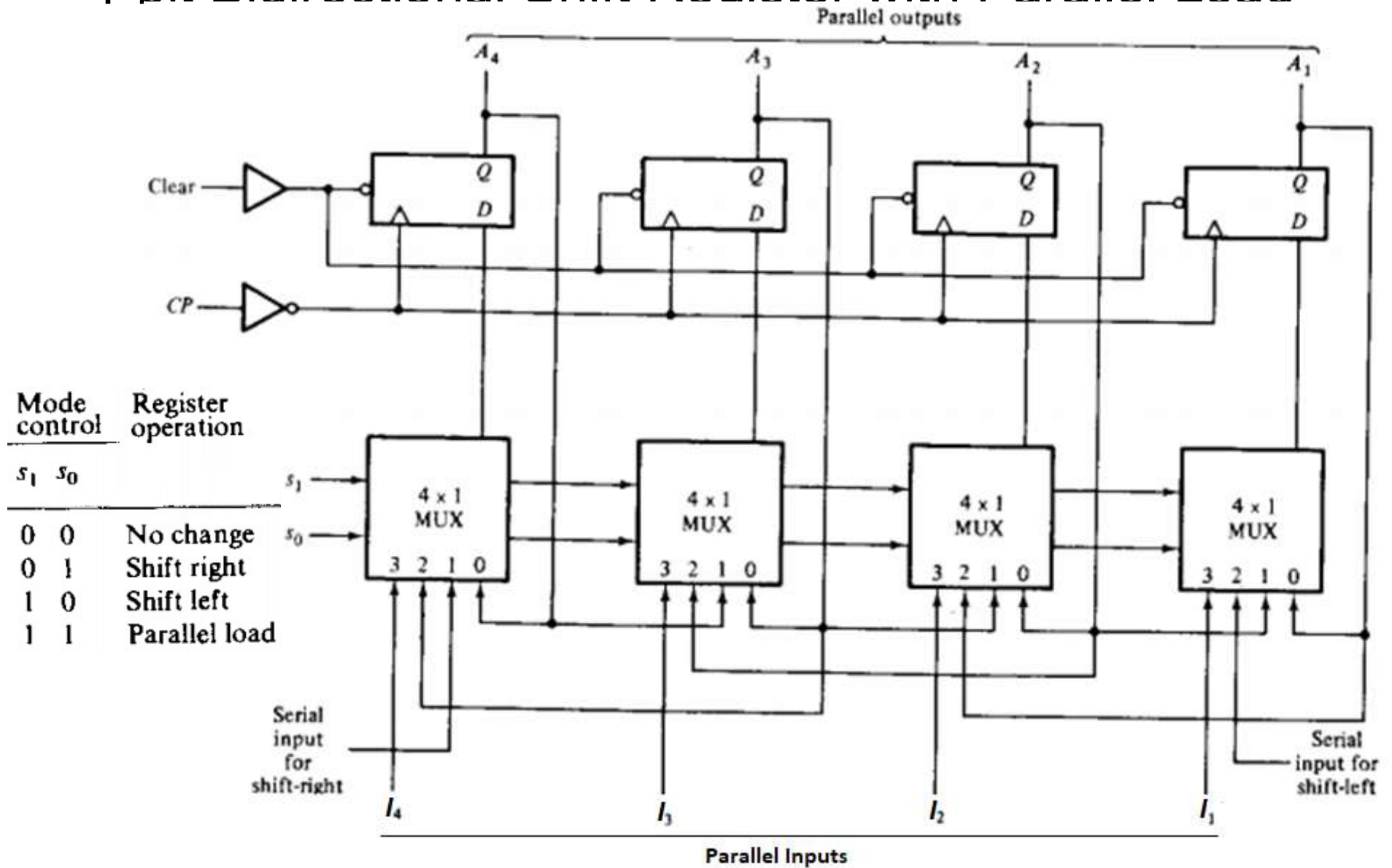
4-bit Bidirectional Shift Register with Parallel Load




Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD Ripple Counter

 - We have already seen the Mod-16 Ripple Counter
- The State Diagram of the BDC Ripple Counter is now given below
- A BCD Counter may also be called a Decade Counter




BCD Ripple Counter (contd.)

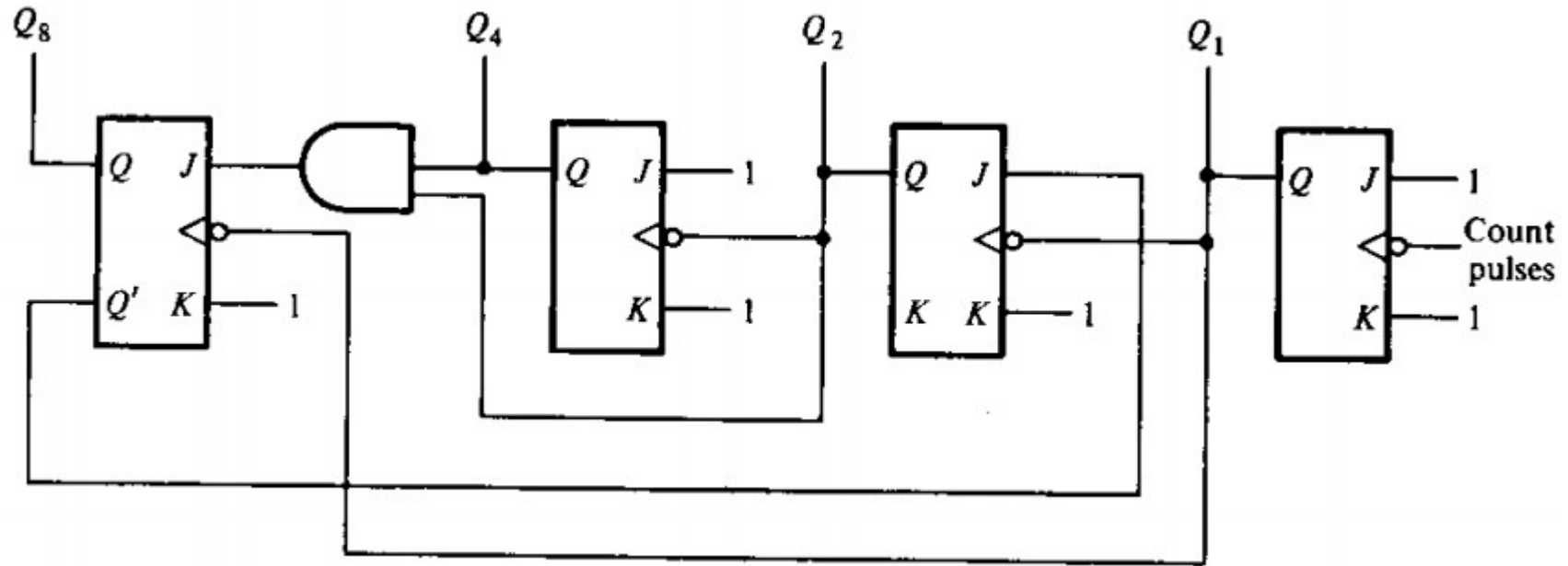

1. Q_1 is complemented on the negative edge of every count pulse.
2. Q_2 is complemented if $Q_8 = 0$ and Q_1 goes from 1 to 0. Q_2 is cleared if $Q_8 = 1$ and Q_1 goes from 1 to 0.
3. Q_4 is complemented when Q_2 goes from 1 to 0.
4. Q_8 is complemented when $Q_4Q_2 = 11$ and Q_1 goes from 1 to 0. Q_8 is cleared if either Q_4 or Q_2 is 0 and Q_1 goes from 1 to 0.


Timing Diagram of the BCD Ripple Counter

 


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

3-Decade Decimal BCD Counter

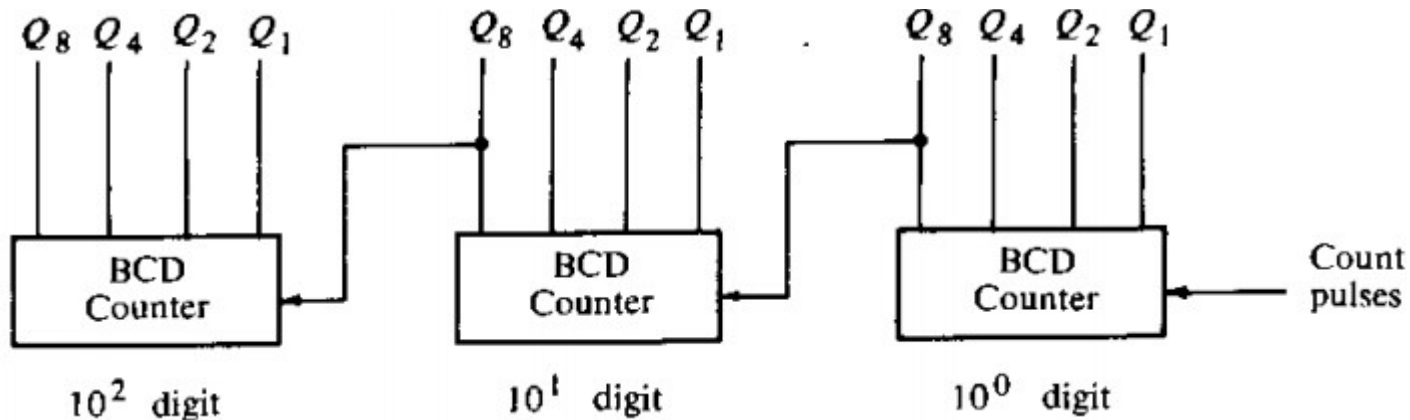- We have seen the asynchronous (ripple) BCD Counter just now
- Design the synchronous BCD counter also
- Using any of the above two, we can design n – Decade Counter
- We can use the BCD-to-7 Segment Decoder at the output of this n – Decade Counter



4-bit Synchronous Binary Counter

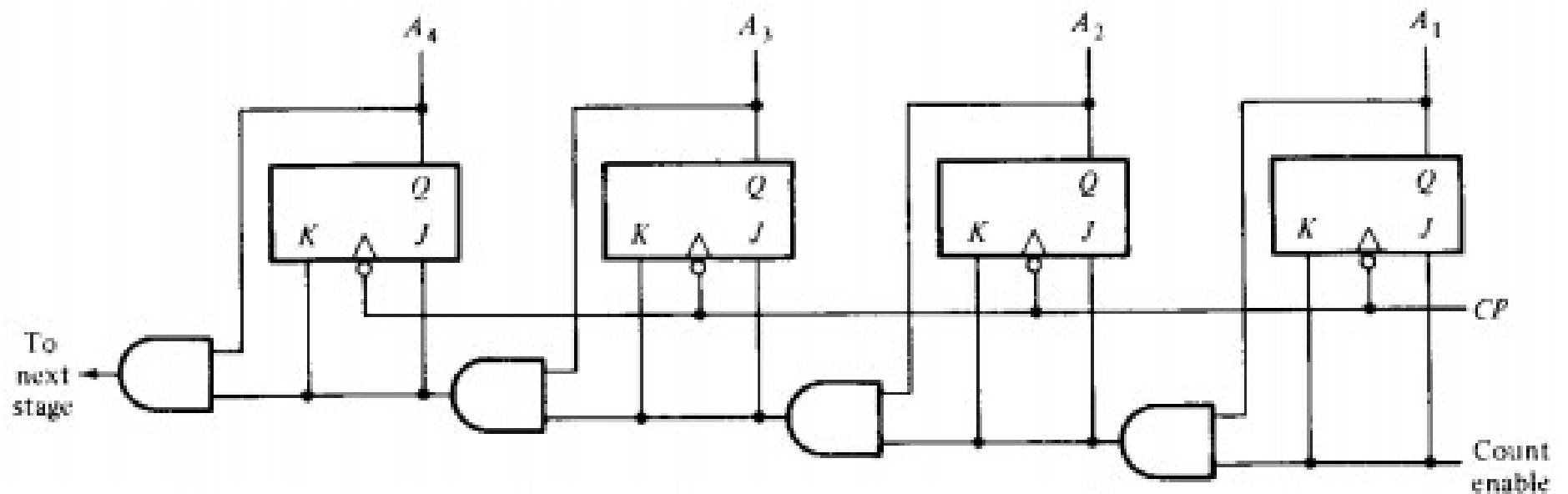


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Binary Count Sequence

A_4	A_3	A_2	A_1
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

4-bit Up-Down Binary Counter

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Synchronous BCD Counter

Count sequence				Flip-flop inputs				Output carry
Q_8	Q_4	Q_2	Q_1	TQ_8	TQ_4	TQ_2	TQ_1	y
0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	1	1	0
0	0	1	0	0	0	0	1	0
0	0	1	1	0	1	1	1	0
0	1	0	0	0	0	0	1	0
0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	0	1	0
0	1	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1	0
1	0	0	1	1	0	0	1	1

$$TQ_1 = 1$$

$$TQ_2 = Q_8'Q_1$$


$$TQ_4 = Q_2Q_1$$

$$TQ_8 = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI


Binary Counter with Parallel Load

 

Clear	CP	Load	Count	Function
0	X	X	X	Clear to 0
1	X	0	0	No change
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Memory Unit

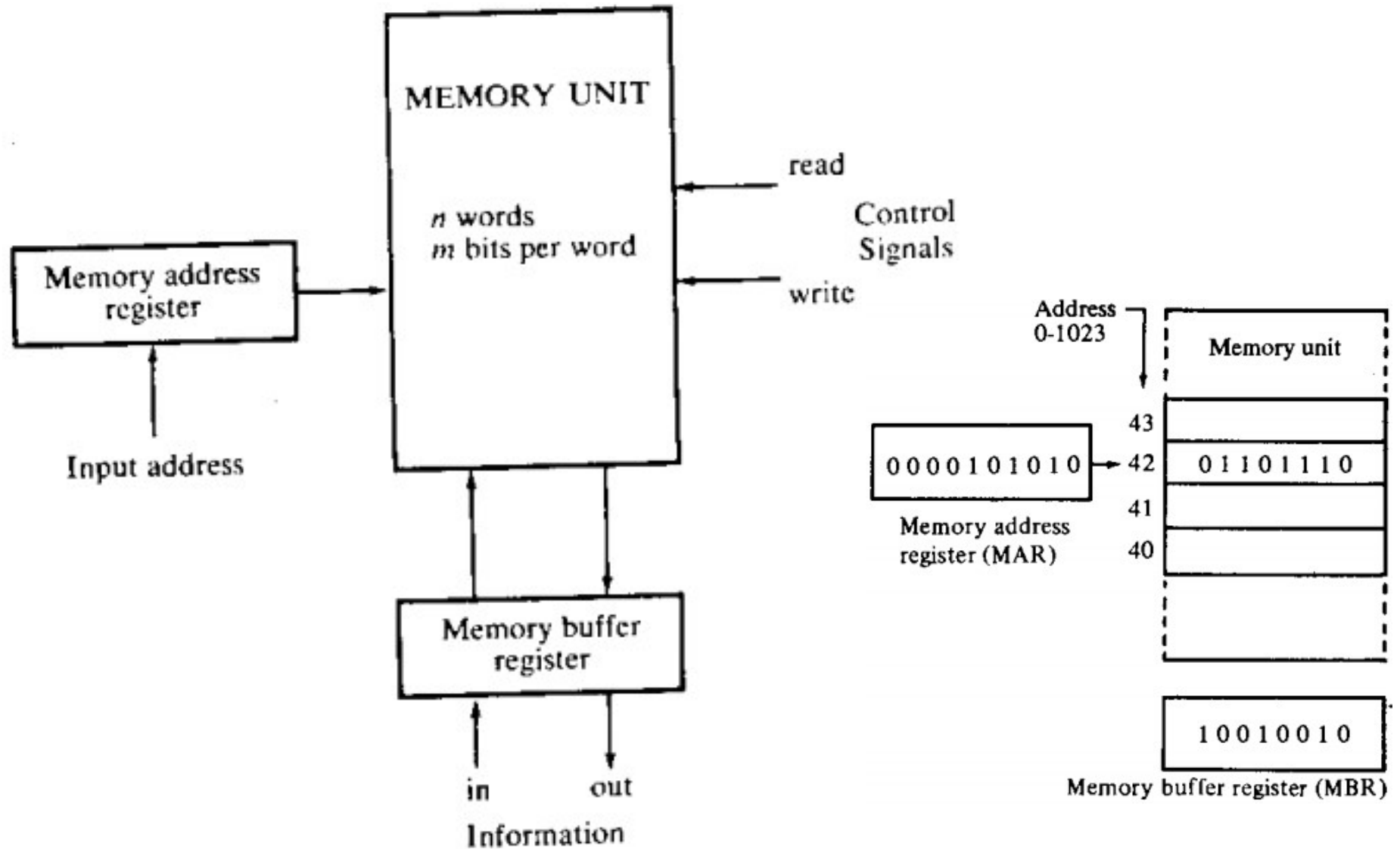


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Memory Cell

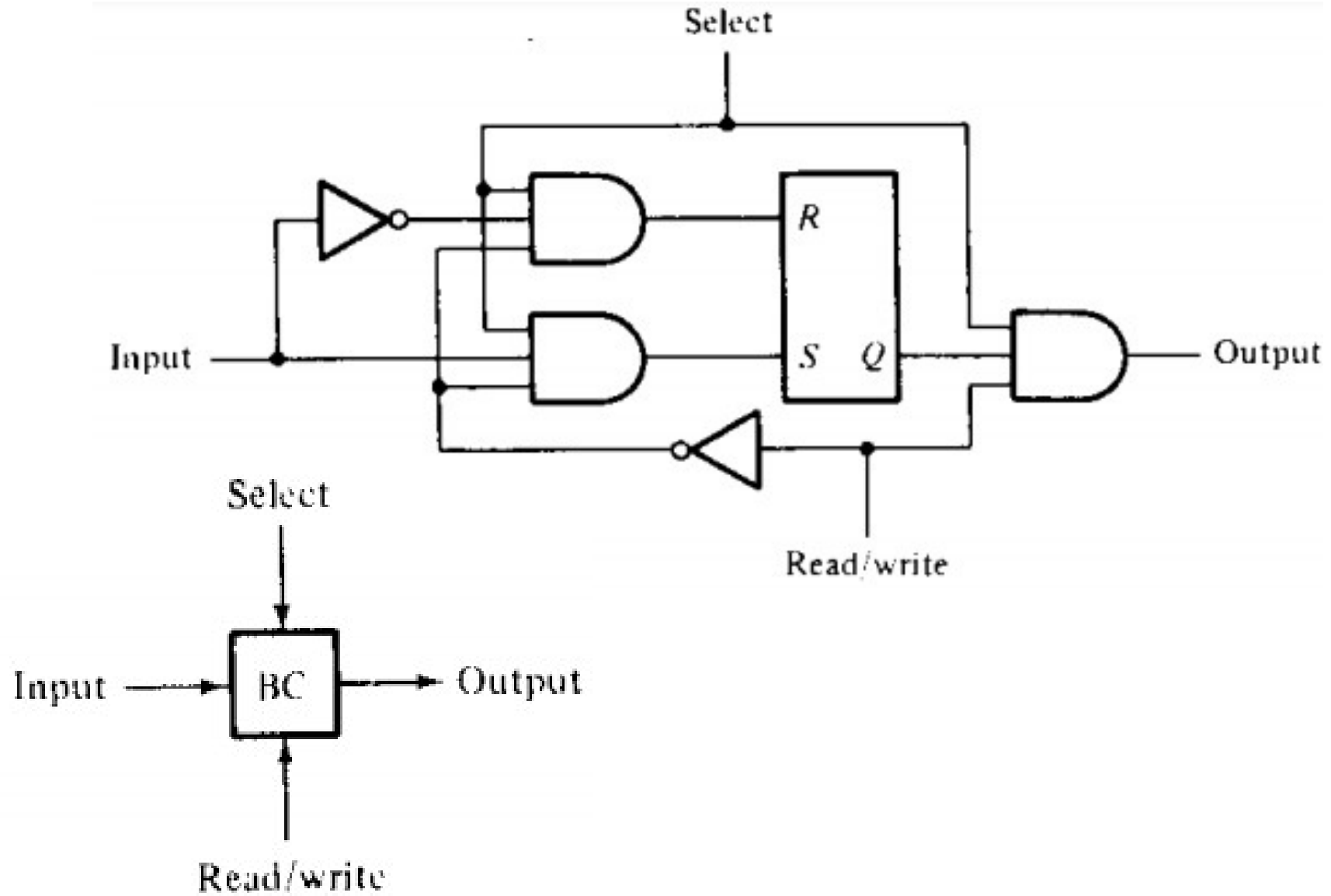

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Memory Organization

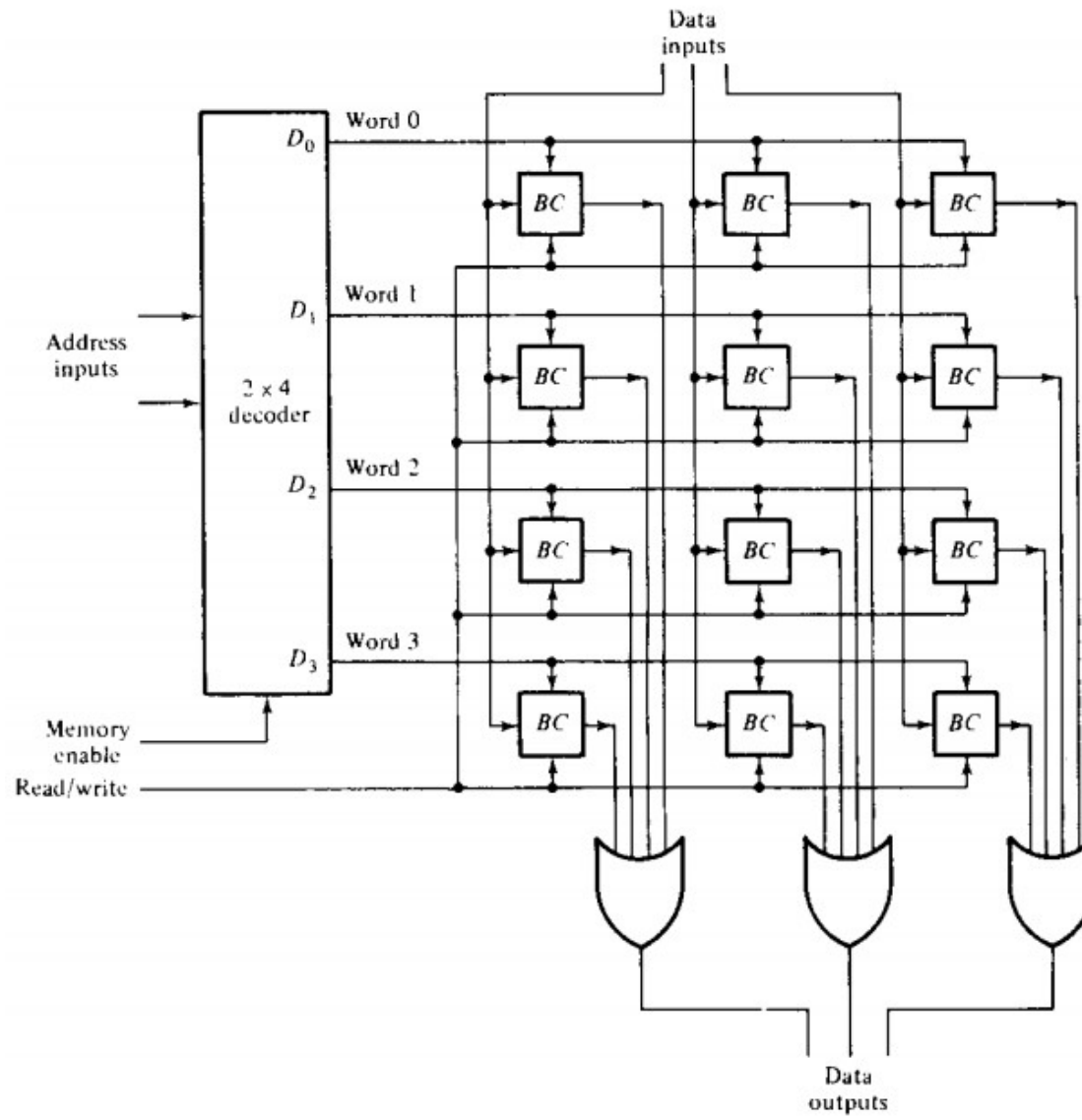

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Unit-III Completed

UNIT III.

SEQUENTIAL LOGIC

Definition and state representation of Flip-Flops, RS, D, JK-M/S, their working characteristics, State Tables, Excitation Tables and triggering. Asynchronous and Synchronous Counters-Design and Analysis, Counter Applications, Description and Operations of Shift Registers, Shift Register/Counters.

Course Outcome

3. Analyse and synthesize digital sequential units.