

COC2070 – Digital Logic and System Design

Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology

Aligarh Muslim University, India

Exclusive OR and Equivalence Functions


Exclusive-OR and equivalence, denoted by \oplus and \odot , respectively, are binary operations that perform the following Boolean functions:

$$x \oplus y = xy' + x'y$$

$$x \odot y = xy + x'y'$$

The two operations are the complements of each other. Each is commutative and associative. Because of these two properties, a function of three or more variables can be expressed without parentheses as follows:
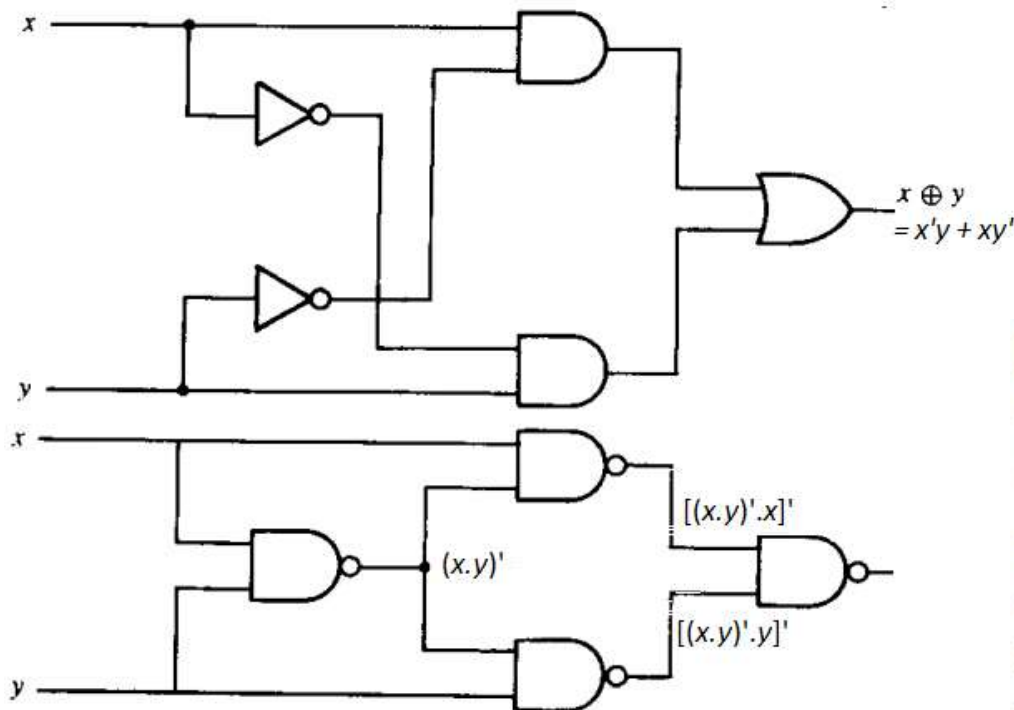
$$(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$$




$$\begin{aligned} & [\{ (x.y)'.x \} . \{ (x.y)'.y \}]' \\ &= \{ (x.y)'.x \} + \{ (x.y)'.y \} \\ &= \{ (x' + y').x \} + \{ (x' + y').y \} \\ &= x.x' + x.y' + x'.y + y'.y' \\ &= 0 + x.y' + x'.y + 0 \\ &= x.y' + x'.y \\ &= x \oplus y \end{aligned}$$

Design of Half Adder


x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = x'y + xy'$$


$$C = xy$$

 


(a) $S = xy' + x'y$
 $C = xy$

 


(b) $S = (x + y)(x' + y')$
 $C = xy$

 

(c) $S = (C + x'y')'$
 $C = xy$

 

 (d) $S = (x + y)(x' + y')$
 $C = (x' + y')'$



(e) $S = x \oplus y$
 $C = xy$

Design of Full Adder



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$x \backslash yz$	00	01	11	10
0		1		1
1	1		1	

$$S = x'y'z + x'yz' + xy'z' + xyz$$


$x \backslash yz$	00	01	11	10
0			1	
1		1	1	1

$$C = xy + xz + yz$$

  

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

 Full Adder with Two Half Adders and an OR Gate



$$S = z \oplus (x \oplus y)$$

$$= z'(xy' + x'y) + z(xy' + x'y)$$

$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= xy'z' + x'yz' + xyz + x'y'z$$

$$C = z(xy' + x'y) + xy = xy'z + x'yz + xy$$

	yz			
	00	01	11	10
x				
0			1	
1		1	1	1

$$C = xy + xz + yz$$

Design of Subtractor

Half-Subtractor

x	y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$$D = x'y + xy'$$

$$B = x'y$$

Full-Subtractor

x	y	z	B	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

	yz			
	00	01	11	10
x				
0		1		1
1	1		1	

$$D = x'y'z + x'yz' + xy'z' + xyz$$

	yz			
	00	01	11	10
x				
0		1	1	1
1			1	

$$B = x'y + x'z + yz$$

COC2070 – Digital Logic and System Design


Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology

Aligarh Muslim University, India

Parallel Adder

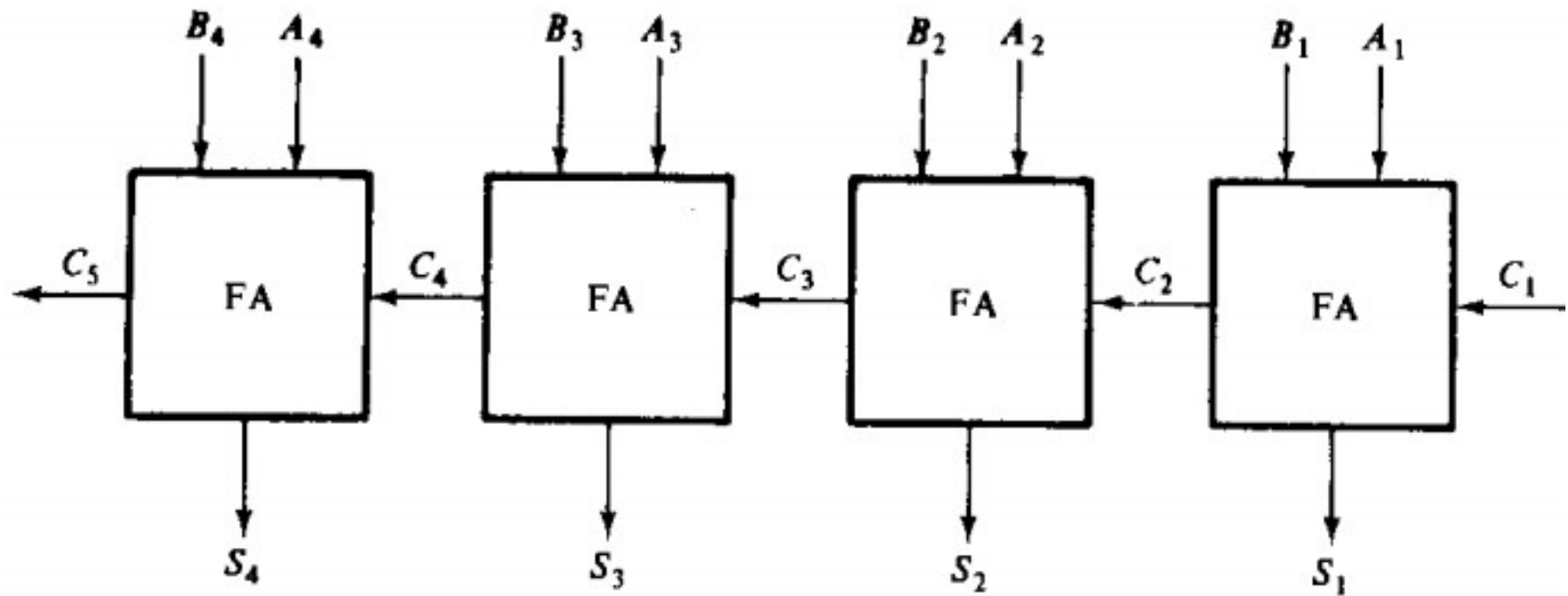

$$\begin{array}{r}
 C_5 \quad C_4 \quad C_3 \quad C_2 \quad C_1 \quad \leftarrow \quad C \\
 A_4 \quad A_3 \quad A_2 \quad A_1 \quad \leftarrow \quad A \\
 + \quad B_4 \quad B_3 \quad B_2 \quad B_1 \quad \leftarrow \quad B \\
 \hline
 S_4 \quad S_3 \quad S_2 \quad S_1 \quad \leftarrow \quad S
 \end{array}$$

$$\begin{array}{r}
 1 \quad 0 \quad 1 \quad 1 \quad \leftarrow \quad C \\
 1 \quad 0 \quad 1 \quad 1 \quad \leftarrow \quad A \\
 + \quad 1 \quad 0 \quad 0 \quad 1 \quad \leftarrow \quad B \\
 \hline
 0 \quad 1 \quad 0 \quad 0 \quad \leftarrow \quad S
 \end{array}$$


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

4-bit Adder/Subtractor

$$\begin{array}{l} x \\ 0 \end{array} \text{ --- } \text{OR} \text{ --- } \begin{array}{l} xy' + x'y \\ = x.1 + x'.0 \\ = x \end{array}$$

$$\begin{array}{l} x \\ 1 \end{array} \text{ --- } \text{OR} \text{ --- } \begin{array}{l} xy' + x'y \\ = x.0 + x'.1 \\ = x' \end{array}$$

$$A + B' + 1 = A - B$$

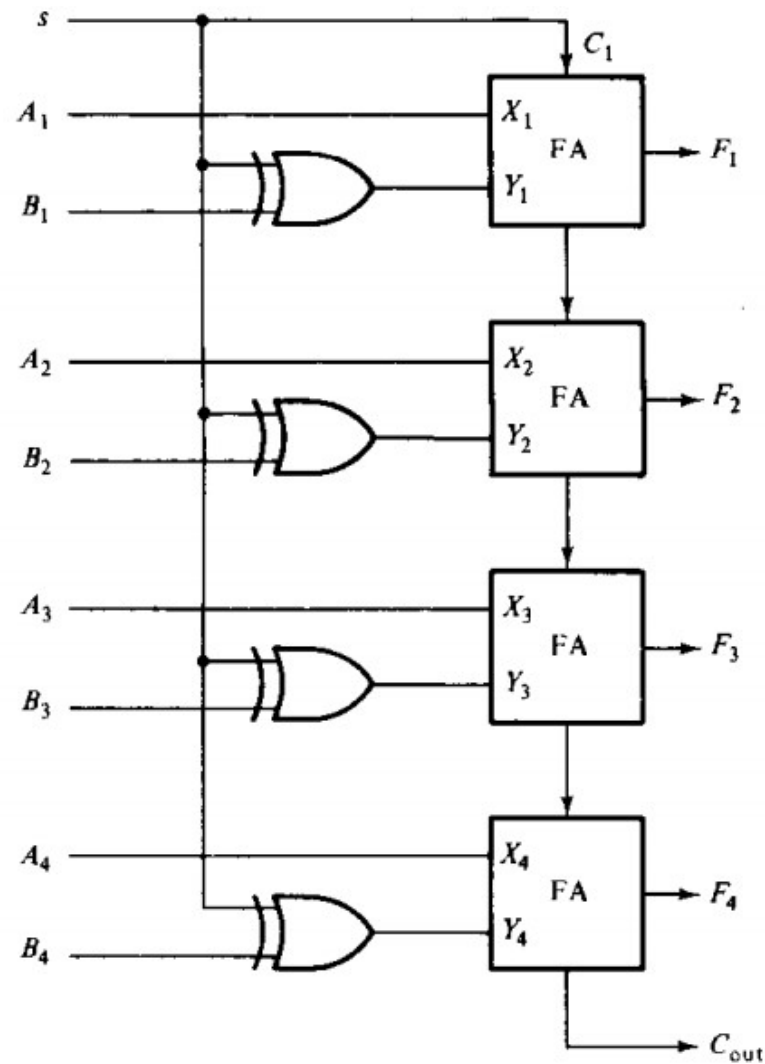

BCD to Excess-3 Code Converter

Input BCD				Output Excess-3 code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

$$z = D'$$


$$y = CD + C'D' = CD + (C + D)'$$

$$\begin{aligned} x &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)' \end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD to Excess-3 Code Converter (contd.)

 


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD to Excess-3 Code Converter (contd.)

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD to Excess-3 Code Converter (contd.)

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD Adder


$$C = K + Z_8Z_4 + Z_8Z_2$$

Binary sum					BCD sum					Decimal
K	Z_8	Z_4	Z_2	Z_1	C	S_8	S_4	S_2	S_1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD Adder (contd.)

$$C = K + Z_8Z_4 + Z_8Z_2$$

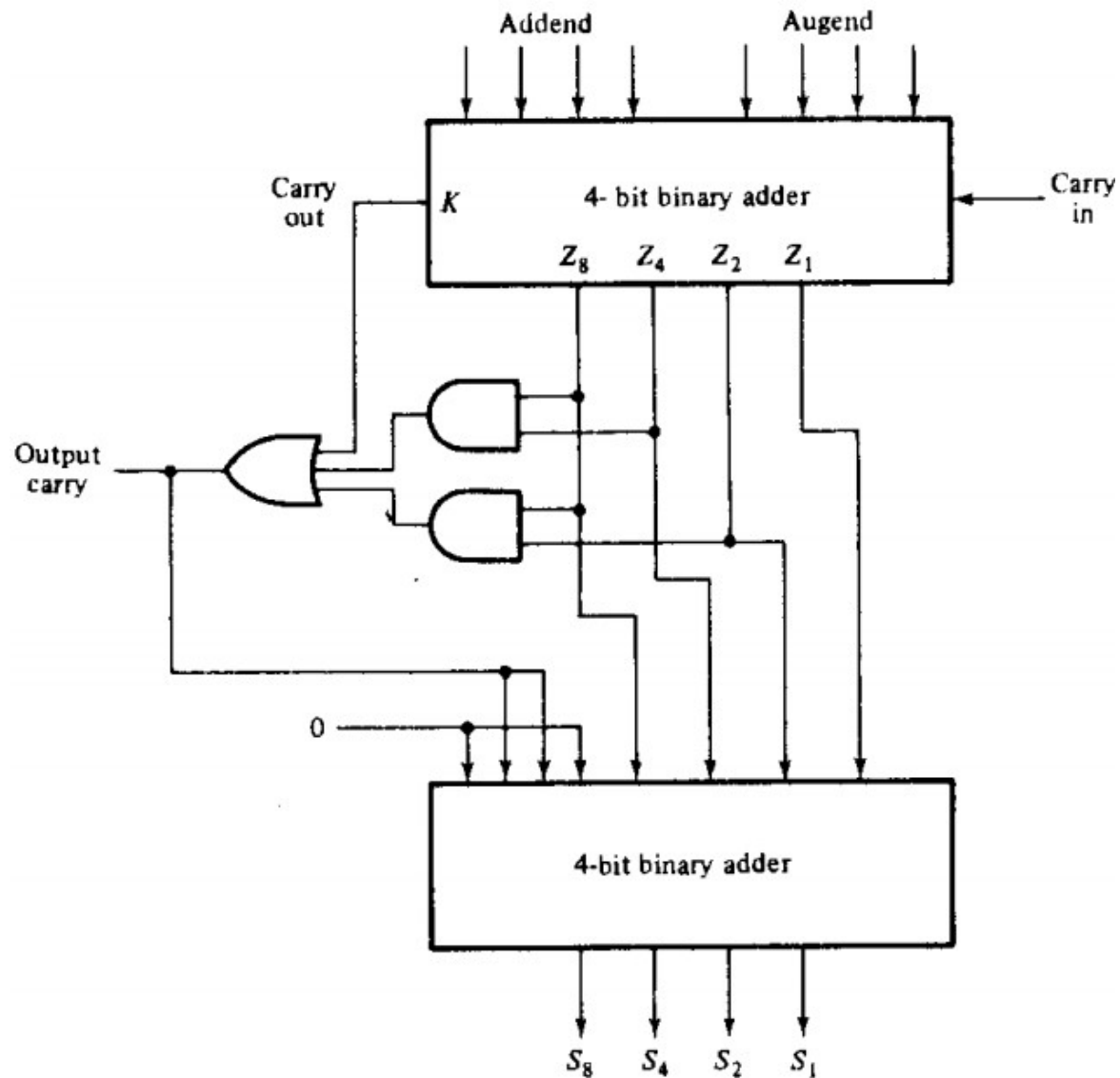

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Magnitude Comparator

$$A = A_3A_2A_1A_0$$

$$B = B_3B_2B_1B_0$$


$$x_i = A_iB_i + A'_iB'_i \quad i = 0, 1, 2, 3$$

$$(A = B) = x_3x_2x_1x_0$$

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

Magnitude Comparator (contd.)

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

COC2070 – Digital Logic and System Design

Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology

Aligarh Muslim University, India

Decoders

Discrete quantities of information are represented in digital systems with binary codes. A binary code of n bits is capable of representing up to 2^n distinct elements of the coded information. A *decoder* is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. If the n -bit decoded information has unused or don't-care combinations, the decoder output will have less than 2^n outputs.


The decoders presented here are called n -to- m line decoders where $m \leq 2^n$. Their purpose is to generate the 2^n (or less) minterms of n input variables.

Truth table of a 3-to-8 line decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

3-to-8 Line Decoder

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD-to-Decimal Decoder

	yz			
	00	01	11	10
wx				
00	D_0	D_1	D_3	D_2
01	D_4	D_5	D_7	D_6
11	X	X	X	X
10	D_8	D_9	X	X

$$D_0 = \underline{w'.x'.y'.z'}$$

$$D_1 = \underline{w'.x'.y'.z}$$

$$D_2 = x'.\underline{y.z'}$$

$$D_3 = x'.\underline{y.z}$$

$$D_4 = \underline{x.y'.z'}$$

$$D_5 = x.\underline{y'.z}$$

$$D_6 = \underline{x.y.z'}$$


$$D_7 = \underline{x.y.z}$$

$$D_8 = \underline{w.z'}$$

$$D_9 = \underline{w.z}$$

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

BCD-to-Decimal Decoder Logic Diagram

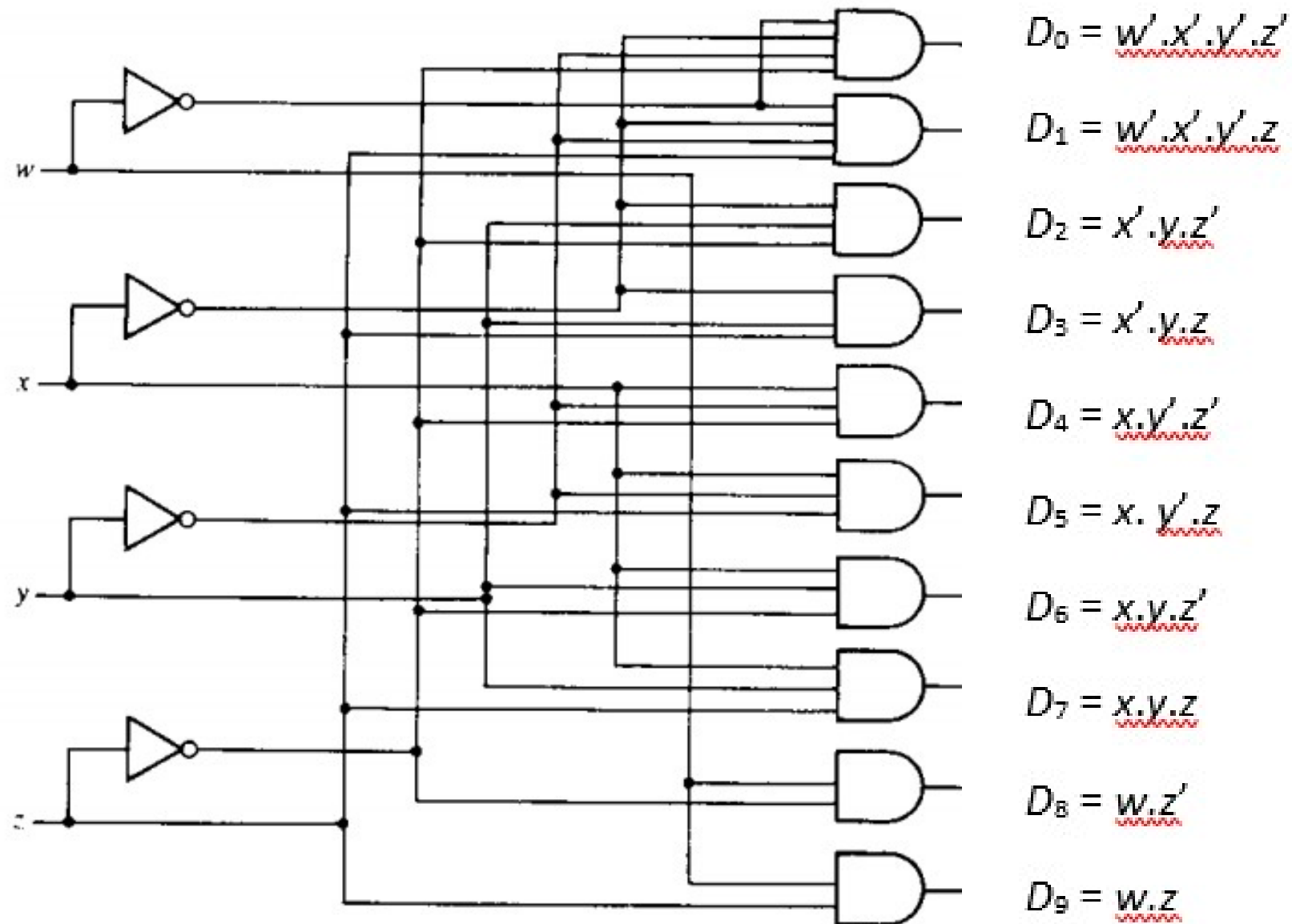


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Realization of Boolean Functions using Decoders

From the truth table of the full-adder, we obtain the functions for this combinational circuit in sum of minterms:


$$S(x, y, z) = \Sigma(1, 2, 4, 7)$$

$$C(x, y, z) = \Sigma(3, 5, 6, 7)$$

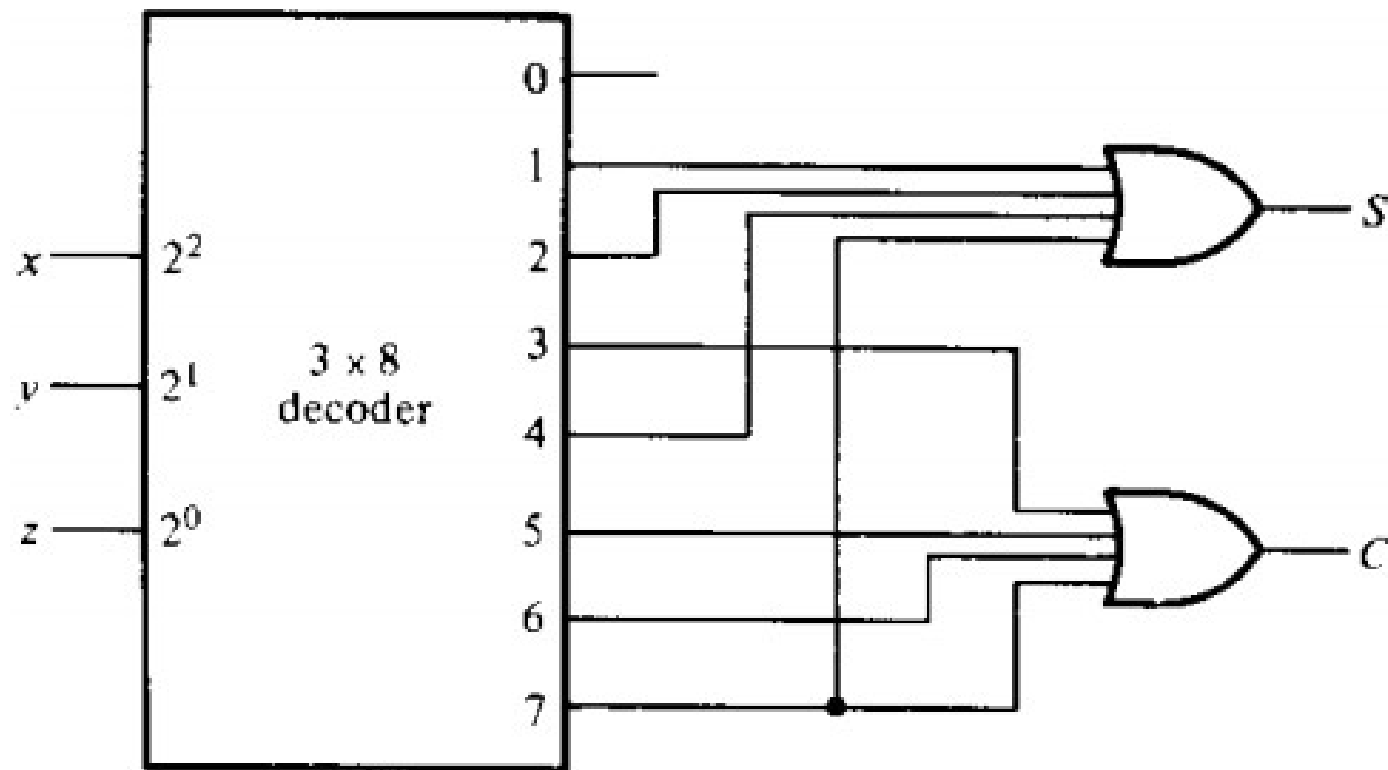


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

DeMultiplexer

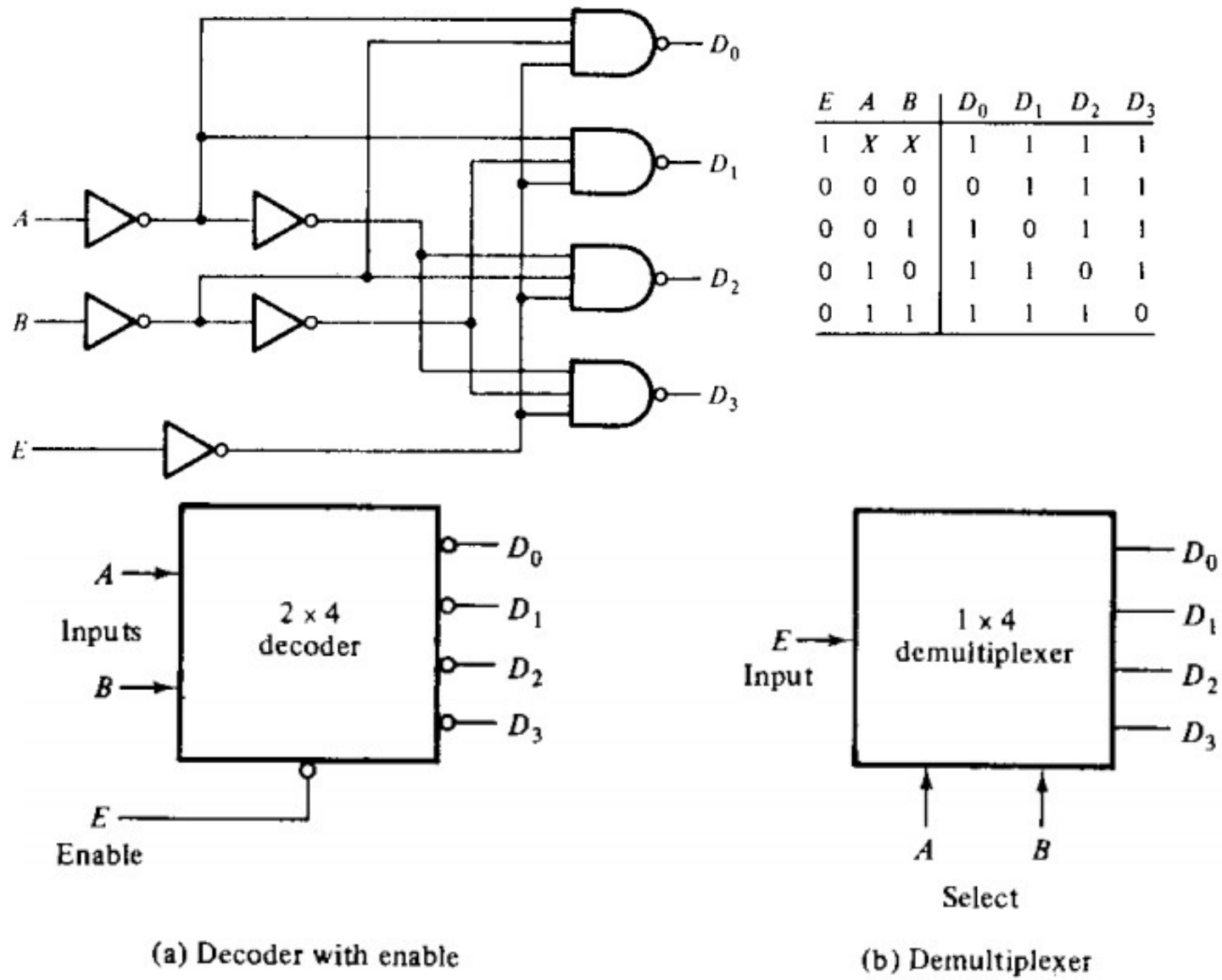

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Higher Order Decoders

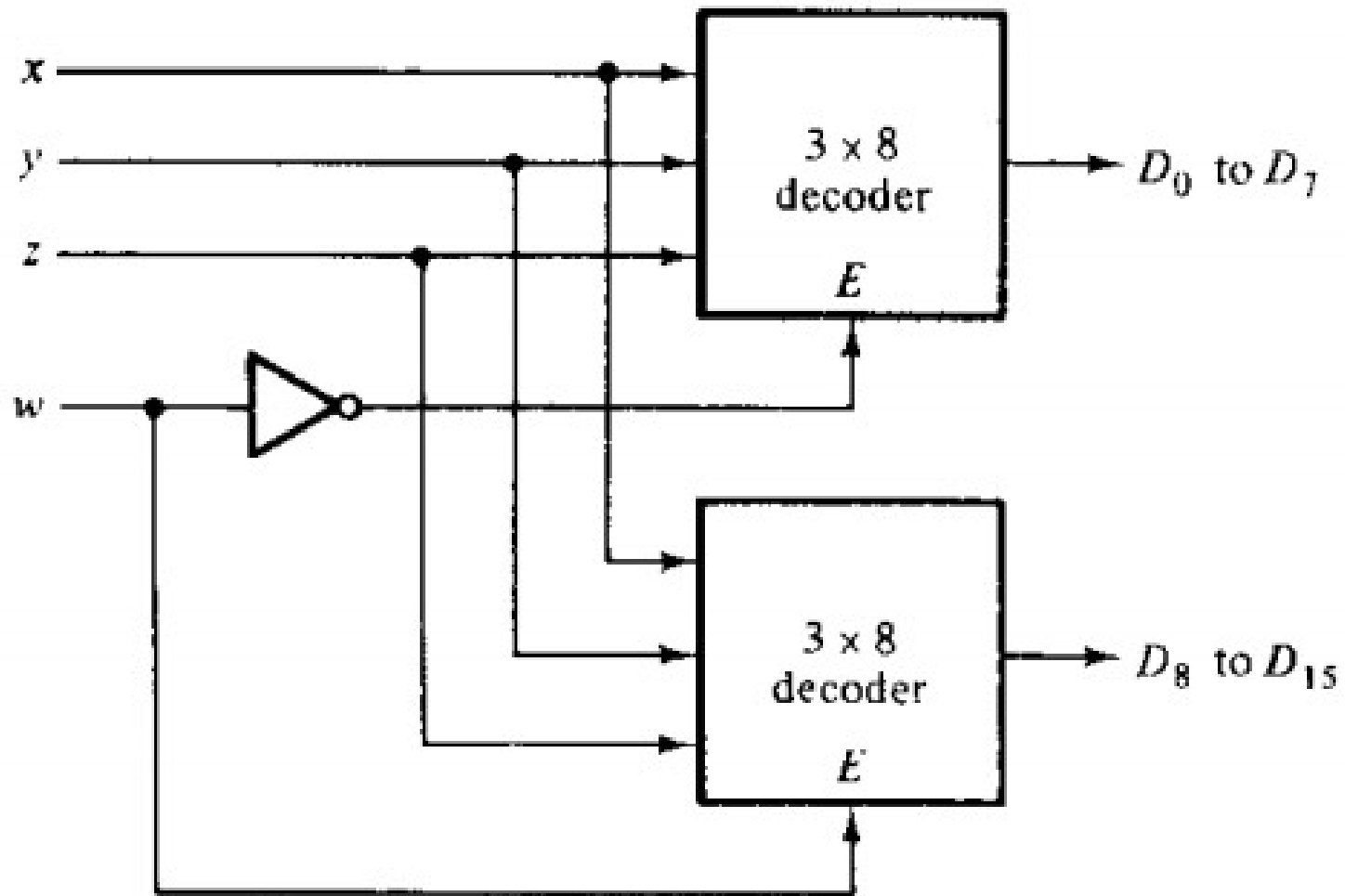

4 × 16 decoder constructed with two 3 × 8 decoders

COC2070 – Digital Logic and System Design

Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology


Aligarh Muslim University, India

Encoders

Truth table of octal-to-binary encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Octal to Binary Encoder

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Priority Encoder


Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
x	1	0	0	0	0	0	0	0	0	1
x	x	1	0	0	0	0	0	0	1	0
x	x	x	1	0	0	0	0	0	1	1
x	x	x	x	1	0	0	0	1	0	0
x	x	x	x	x	1	0	0	1	0	1
x	x	x	x	x	x	1	0	1	1	0
x	x	x	x	x	x	x	1	1	1	1

$$x = D_4 D_5' D_6' D_7' + D_5 D_6' D_7' + D_6 D_7' + D_7$$


$$y = D_2 D_3' D_4' D_5' D_6' D_7' + D_3 D_4' D_5' D_6' D_7' + D_6 D_7' + D_7$$

$$z = D_1 D_2' D_3' D_4' D_5' D_6' D_7' + D_3 D_4' D_5' D_6' D_7' + D_5 D_6' D_7' + D_7$$

Multiplexers

 

(a) Logic diagram

 

(c) Block diagram


s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

A 4-to-1 line multiplexer

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Quadruple 2-to-1 Line Multiplexers

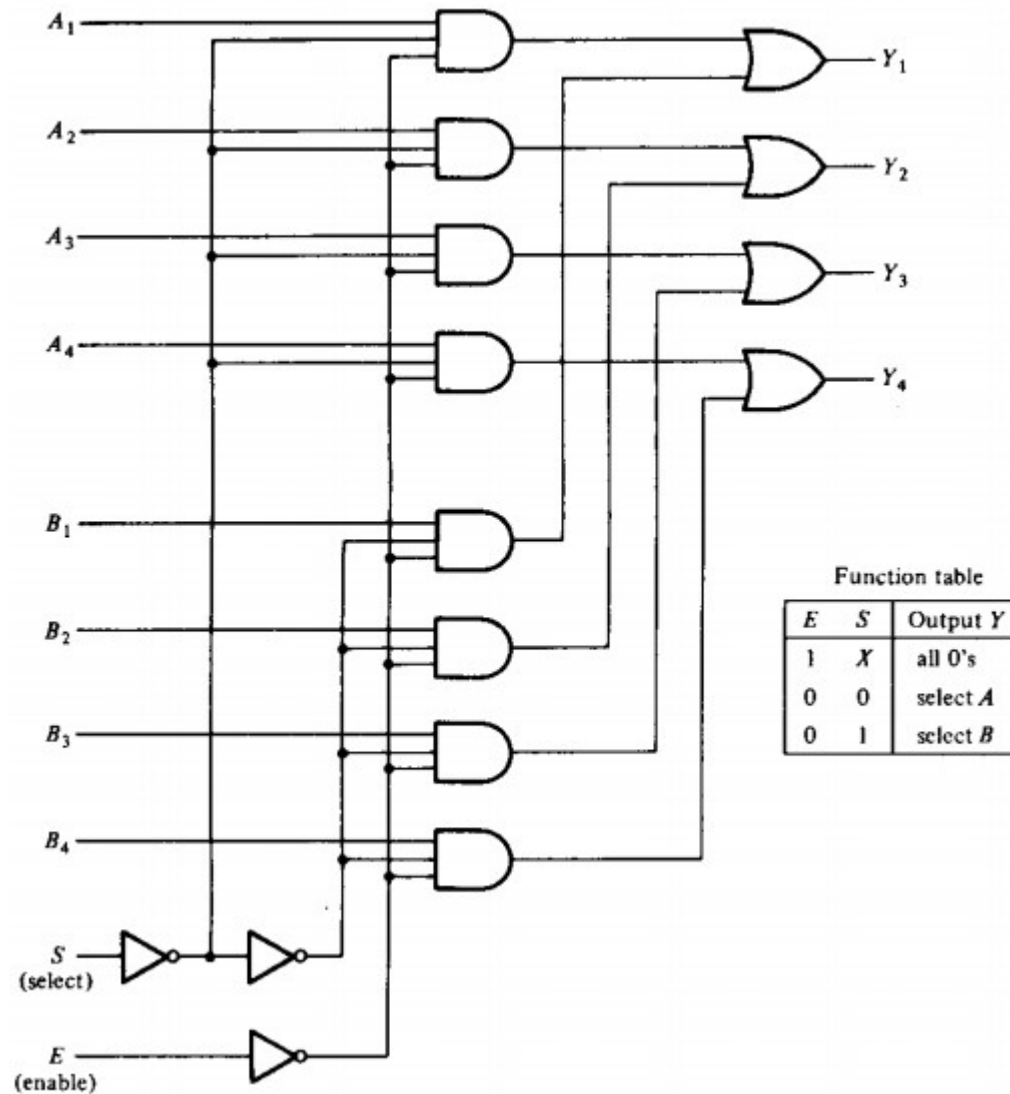


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Function Implementation Using Multiplexers

$$F(A, B, C) = \Sigma(1, 3, 5, 6)$$


Minterm	<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

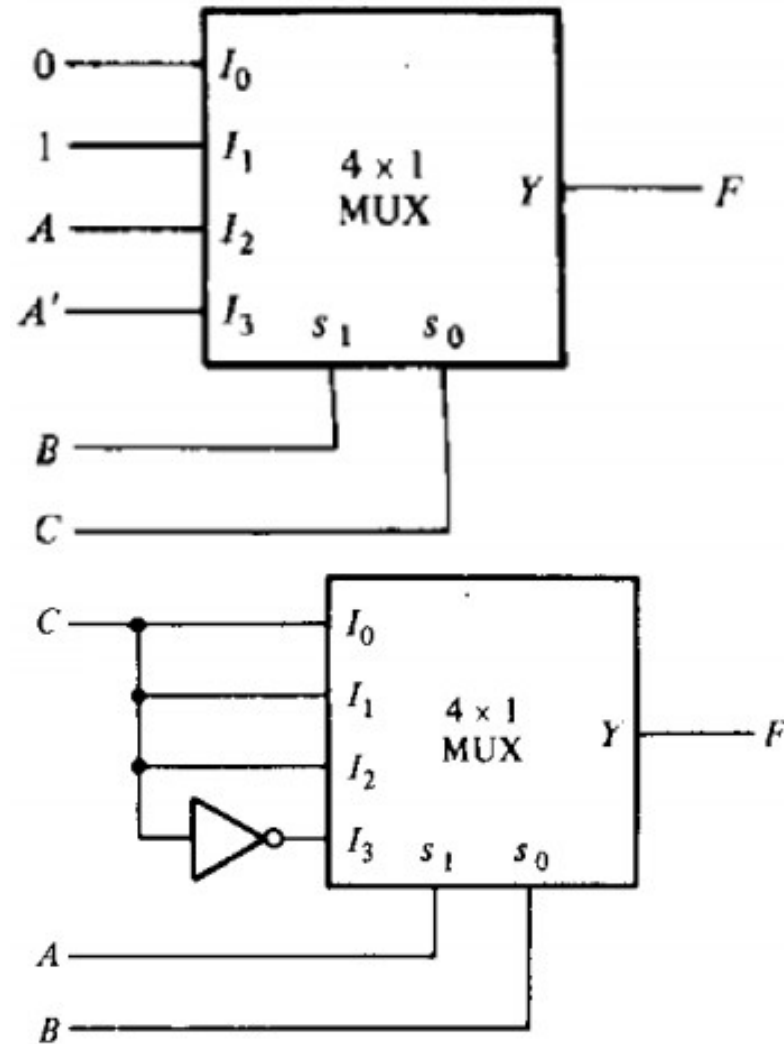

Function Implementation Using Multiplexers

$$F(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 

- Only Canonical SOP form functions are implemented
- One function per multiplexer
- No external gate required

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

COC2070 – Digital Logic and System Design




Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology


Aligarh Muslim University, India

Higher Order MUX using Lower Order MUXes

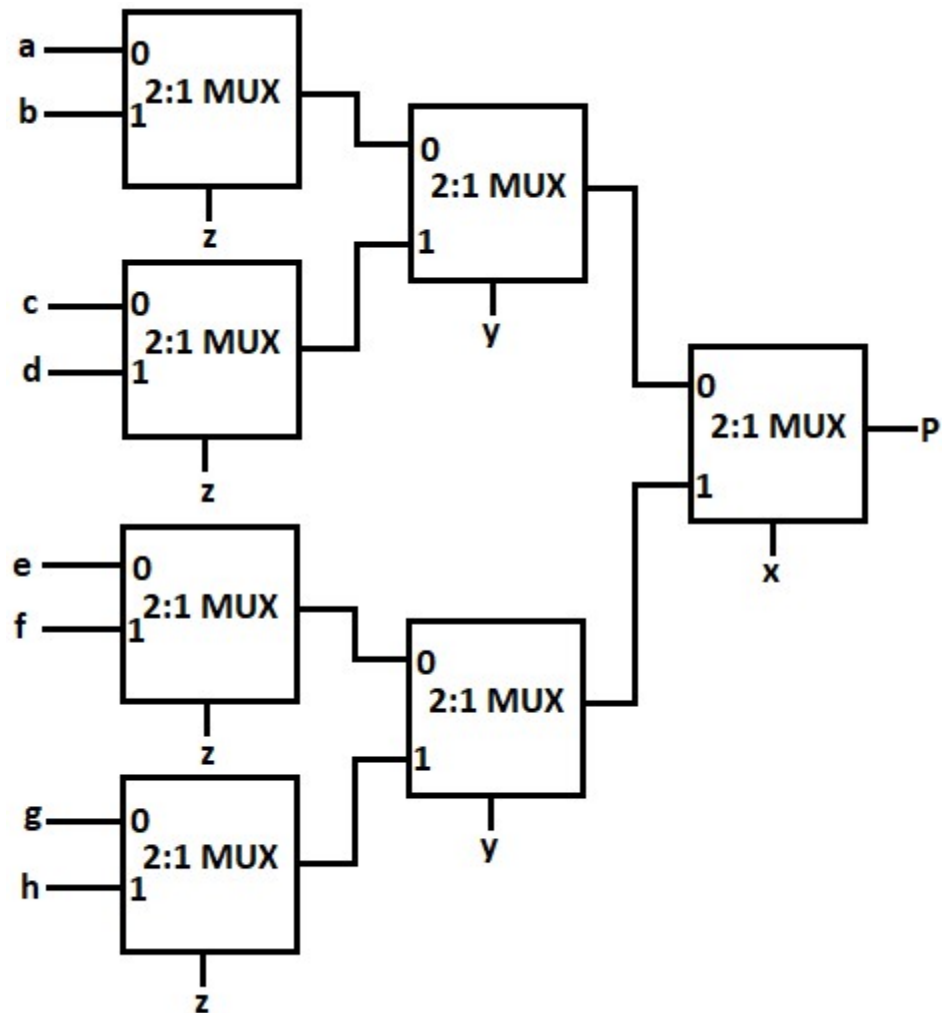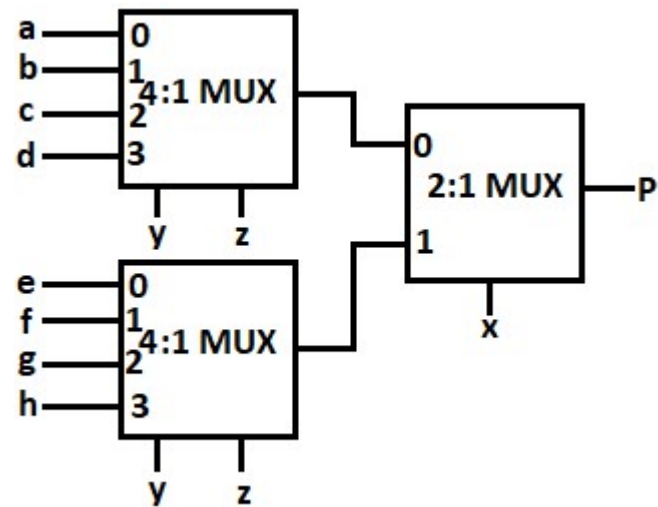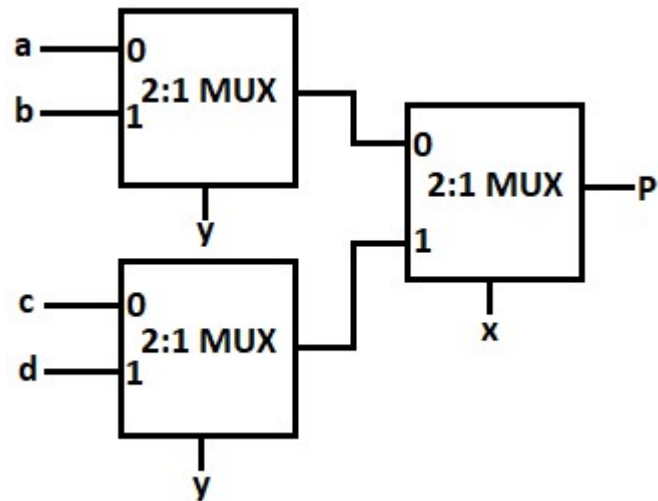


Read Only Memory (ROM)

 - Decoder followed by Encoder
- Non-volatile



32 × 4 ROM

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

COC2070 – Digital Logic and System Design

Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology

Aligarh Muslim University, India

ROM Applications


- Memory which is non-volatile
- Function Implementation
 - Many functions without any external gate
- Code Converter
 - Decoder followed by encoder
- Look up table
 - e.g. Multiplication tables, log tables, trigonometric tables, etc.
- Waveform Generation
 - Irregular but periodic waveforms
- Boot ROM as it is non-volatile

Function Implementation using ROM


$$F_1(A_1, A_0) = \Sigma(1, 2, 3)$$

$$F_2(A_1, A_0) = \Sigma(0, 2)$$

A_1	A_0	F_1	F_2
0	0	0	1
0	1	1	0
1	0	1	1
1	1	1	0

 


ROM with
AND-OR
Gates

 

ROM With
AND-OR-INVERT
Gates


BCD to Excess-3 Code Converter using ROM

Input BCD				Output Excess-3 code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

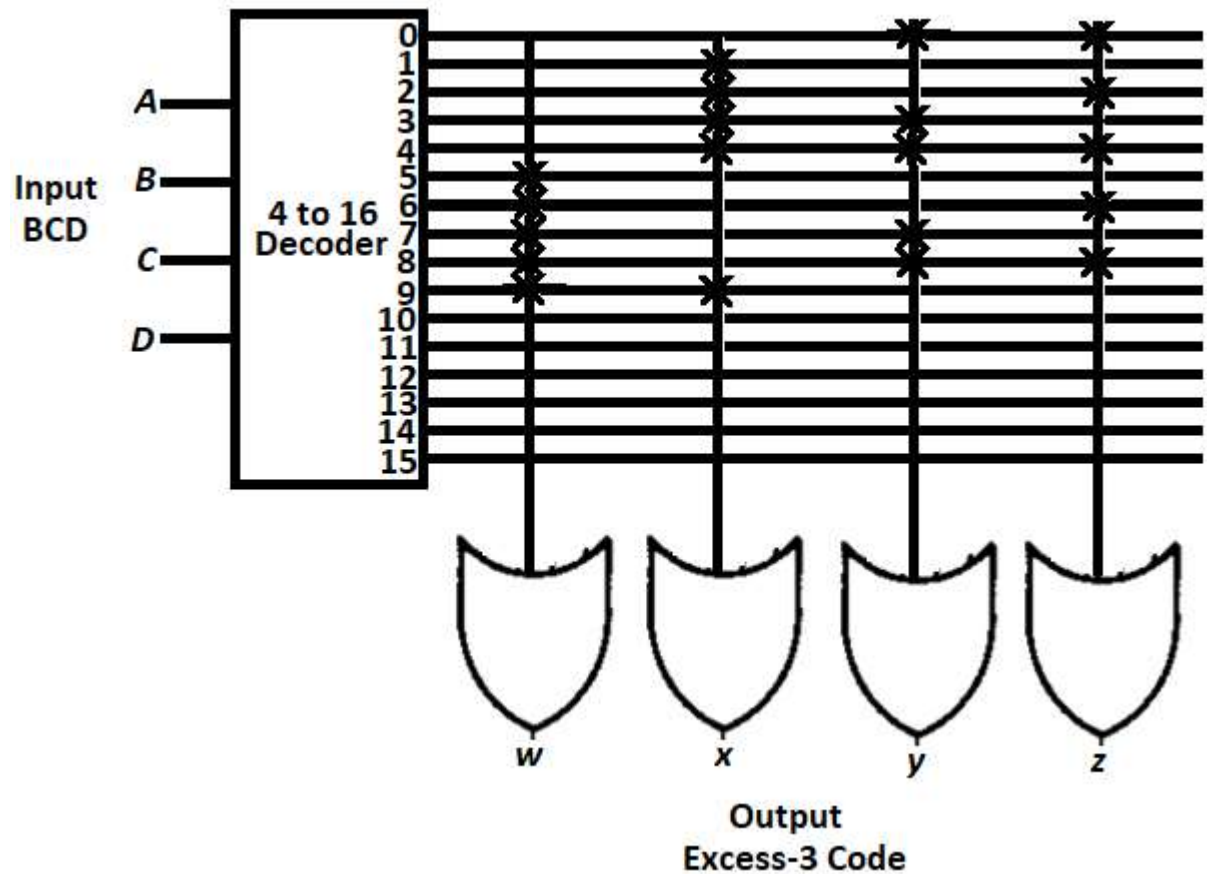

Look-up Table Example: Multiplication Table of 3

Input (Multiplication Factor)		Output (Product)	
Decimal	Binary (a,b,c,d)	Binary (A,B,C,D,E)	Decimal
1	0 0 0 1	0 0 0 1 1	3
2	0 0 1 0	0 0 1 1 0	6
3	0 0 1 1	0 1 0 0 1	9
4	0 1 0 0	0 1 1 0 0	12
5	0 1 0 1	0 1 1 1 1	15
6	0 1 1 0	1 0 0 1 0	18
7	0 1 1 1	1 0 1 0 1	21
8	1 0 0 0	1 1 0 0 0	24
9	1 0 0 1	1 1 0 1 1	27
10	1 0 1 0	1 1 1 1 0	30

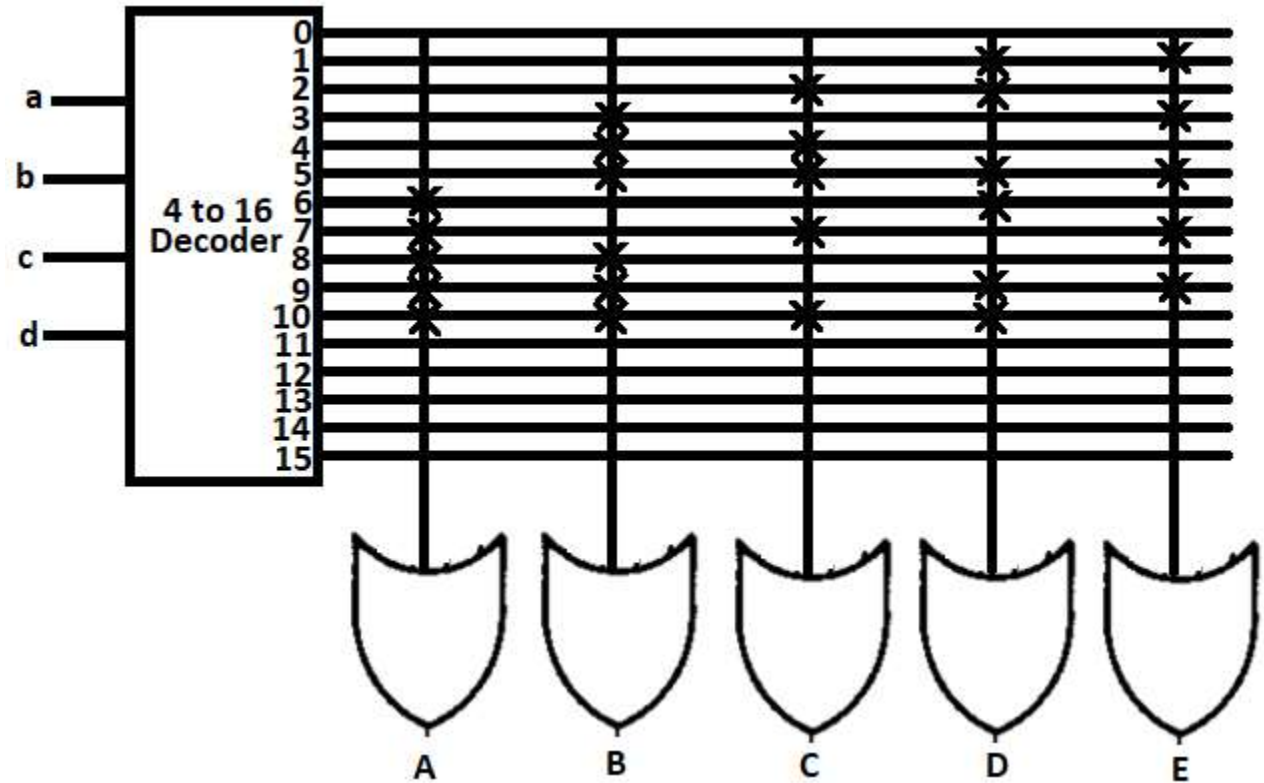


Types of ROM

- ROM : Read Only Memory
 - Programmed in the factory
- PROM: Programmable Read Only Memory
 - May be programmed in the field
- EPROM: Erasable Programmable Read Only Memory
 - Erasure through Ultraviolet exposure
- EEPROM or E²PROM: Electrically Erasable Programmable Read Only Memory
 - Erasure also through electrical signal
- Versatility keeps going up and so is the cost


Programmable Logic Array (PLA)

 - Both AND array as well as OR array is programmable
- Block Diagram of PLA



Example of PLA

$$F_1 = AB' + AC, \quad F_2 = AC + BC$$

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

COC2070 – Digital Logic and System Design

Prof. M. M. Sufyan Beg

Department of Computer Engineering

Z. H. College of Engineering & Technology

Aligarh Muslim University, India

PLA Implementation

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7), F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

	BC 00	01	11	10
A				
0			1	
1		1	1	1

$$F_1 = AC + AB + BC$$

	BC 00	01	11	10
A				
0	0	0		0
1	0			

$$F_1' = B'C' + A'C' + A'B'$$

	BC 00	01	11	10
A				
0	1			1
1	1		1	

$$F_2 = B'C' + A'C' + ABC$$


	BC 00	01	11	10
A				
0		0	0	
1		0		0

$$F_2' = B'C + A'C + ABC'$$

PLA program table


Product term	Inputs			Output	
	A	B	C	F_1	F_2
$B'C'$	1	0	0	1	1
$A'C'$	2	0	0	1	1
$A'B'$	3	0	0	1	—
ABC	4	1	1	—	1
				C	T
				T/C	

PLA Implementation (continued)

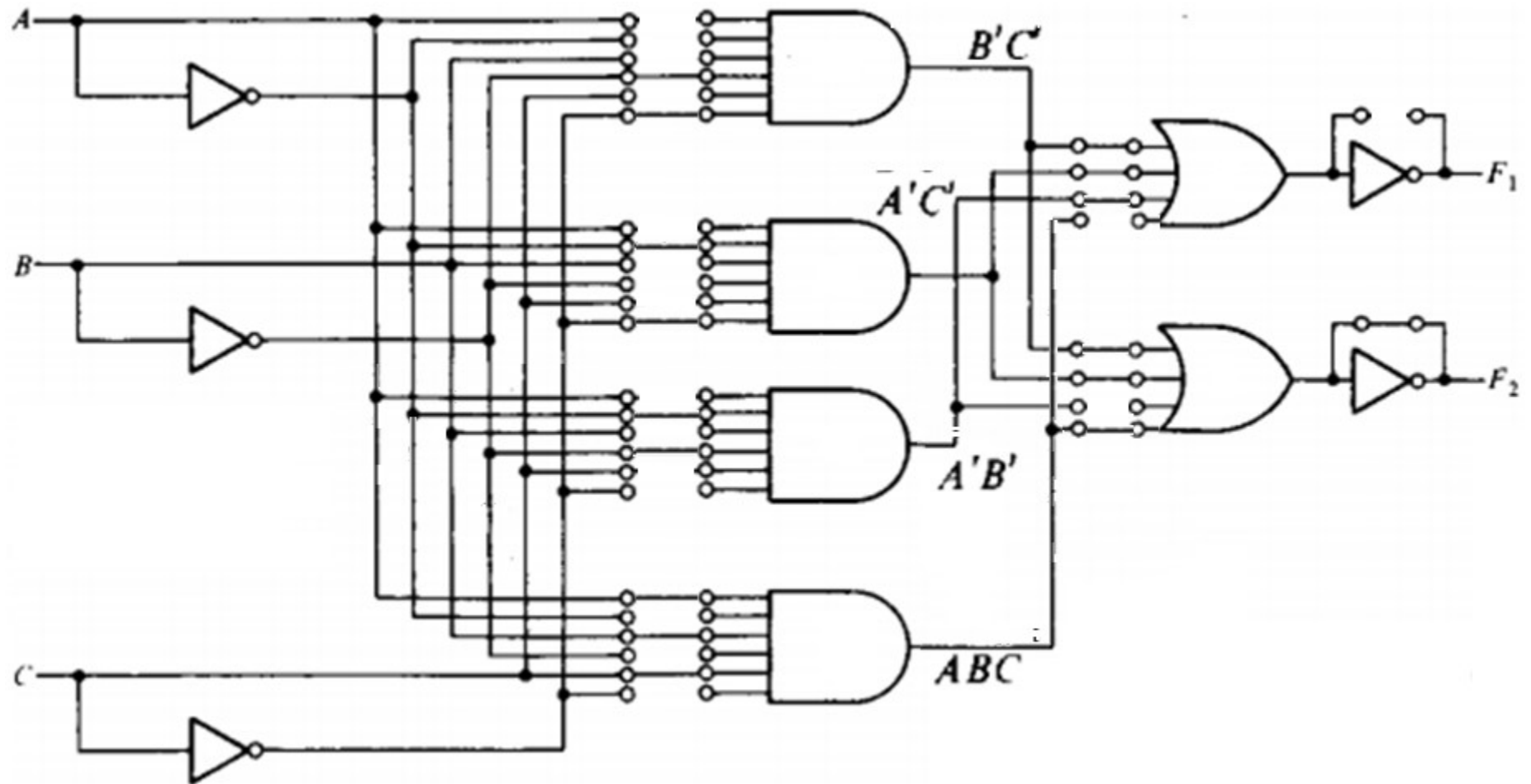

$$F_1 = (B'C' + A'C' + A'B')', \quad F_2 = B'C' + A'C' + ABC$$

Line Diagram of the PLA

 


$$F_1 = (B'C' + A'C' + A'B')', \quad F_2 = B'C' + A'C' + ABC$$

Parity Generator/Checker

Odd-parity generation

Three-bit message			Parity bit generated
x	y	z	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 


Odd-parity check

Four-bits received				Parity-error check
x	y	z	P	C
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Parallel Adder (Ripple Adder)

 


$$\begin{array}{r}
 C_5 \quad C_4 \quad C_3 \quad C_2 \quad C_1 \quad \leftarrow \quad C \\
 A_4 \quad A_3 \quad A_2 \quad A_1 \quad \leftarrow \quad A \\
 + \quad B_4 \quad B_3 \quad B_2 \quad B_1 \quad \leftarrow \quad B \\
 \hline
 S_4 \quad S_3 \quad S_2 \quad S_1 \quad \leftarrow \quad S
 \end{array}$$

$$\begin{array}{r}
 1 \quad 0 \quad 1 \quad 1 \quad \leftarrow \quad C \\
 1 \quad 0 \quad 1 \quad 1 \quad \leftarrow \quad A \\
 + \quad 1 \quad 0 \quad 0 \quad 1 \quad \leftarrow \quad B \\
 \hline
 0 \quad 1 \quad 0 \quad 0 \quad \leftarrow \quad S
 \end{array}$$

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Carry Look Ahead Adder

 

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 C_1) = G_2 + P_2 G_1 + P_2 P_1 C_1$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 C_1$$


Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

 Logic Diagram of a Carry Look Ahead Generator



Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

4-bit Full Adders with Look Ahead Carry

 

Reference: M. Morris Mano, "Digital Logic and Computer Design", PHI

Unit-II Completed

UNIT II.

COMBINATIONAL LOGIC

Hardware aspect of arithmetic logic functions, Half-Adder, Full-Adder, Binary Adder/Subtractor, Parallel Adder, Magnitude Comparator, Demultiplexer, Multiplexer, Parity Checker/Generator, ROM, etc.

Course Outcome

2. Analyse and synthesize digital combinational units.